
Seat No.:	Enrolment No.
-----------	---------------

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-IV EXAMINATION - SUMMER 2016

Subject Code:141101		ect Code:141101	Date:03/06/2016	
	Subj	ect Name:Advance Electronics		
	Time:10:30 AM to 01:00 PM		Total Marks: 70	
	Instru			
		 Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. 		
Q.1	(a)	Compare different types of power amplifier based on composition of Q-point, efficiency, distortion, and application	-	0′
	(b)	For Dual slop integrator type ADC 1 Draw basic circuit 2 Explain its working 3 List its advantages over other type of ADCs. 4 List it's applications		0'
Q.2		Draw the hybrid $-\pi$ model for a transistor in CE configuration Derive the equation for transconductance g_m .		0'
	(b)	Draw the block diagram of operational amplifier and ex OR		0'
	(b)	Draw op-amp based Wien bridge oscillator. Obtain freq discuss amplitude stabilization for the same.	uency of oscillation and	0'
Q.3	(a)	What are the fundamental different between an amplifier and oscillator? Explain concept of oscillation with Barkhausen criteria.		0′
	(b)	A 5-bit R-2R ladder network with logic '0'=0V and logic i) Analog output due to LSB change ii) Full scale output voltage iii) Analog output for digital input 11100. OR	'1'=5V. Find	0'
Q.3	(a)	Explain voltage series, voltage shunt, current series an in brief.	d current shut feedback	0
	(b)	Write a short note on two stage RC-coupled amplifier.		0'
Q.4	(a)	Explain cascaded amplifier and also derive the expression decibels of an n-stage cascaded amplifier and why to	_	0′
	(b)	Describe the operation of successive approximation AD OR		0'
Q.4	(a) (b)	Explain Clapp oscillator using transistor and FET. Determine the voltage gain, input, and output impedance with feedback for voltage series feedback having A= -100, R_i = 10 k Ω , R_0 =20k Ω for feedback of i) β =0.1 and ii) β = -0.5.		0':
Q.5	(a)	For the signal and circuit of figure below, determine t that may be used. Op-amp slew rate is $SR = 0.5 \text{ V/}\mu\text{s}$.	he maximum frequency	0′

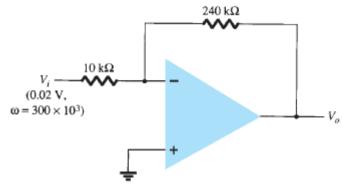

(b) Draw and explain the working principle of crystal controlled oscillator.

OR

Q.5 (a) Sketch the circuit of a crystal controlled oscillator.

(b) Tabled the compare of TTL,CMOS, and ECL logic families based on speed, fan-in, fan-out, noise immunity, power dissipation, and application.
