Enrol	ment	No.	

		GUJARAT TECHNOLOGICAL UNIVERSITY	
BE - SEMESTER-V- EXAMINATION – SUMMER 2016 Subject Code: 150903 Date: 09			16
	•	ct Name: Power Electronics - I	10
Т	ime	: 02:30 PM to 05:00 PM Total Marks:	70
I	nstruc		
		<ol> <li>Attempt all questions.</li> <li>Make suitable assumptions wherever necessary.</li> </ol>	
		3. Figures to the right indicate full marks.	
Q.1	(a)	Explain GTO turn on and turn off characteristics.	07
C C	<b>(b)</b>	Explain working of Cuk converter with schematic diagram and waveforms.	07
Q.2	(a)	Discuss two transistor analogy of SCR.	07
	<b>(b</b> )	Discuss static characteristics of IGBT. Compare IGBT with MOSFET.	07
		OR	
	<b>(b</b> )	Mention requirements of Gate circuit. Discuss use of DIAC in firing circuit.	07
Q.3	(a)	Discuss thermal model of thyristor. Write steps to design a snubber circuit.	07
	<b>(b</b> )	Discuss effect of source and load inductances on the performance of AC to DC controlled converter.	07
		OR	
Q.3	(a) (b)	Why thyristors are connected in series? Discuss series operation of thyristor. Discuss power factor improvement techniques used in AC to DC controlled	07 07
	(U)	converter.	07
Q.4	<b>(a)</b>	Discuss four quadrant operations of DC drives.	07
	<b>(b</b> )	Explain working of buck-boost converter with schematic diagram and waveforms.	07
		OR	
Q.4	(a)	Explain working of Jone's chopper with schematic diagram and waveforms.	07
	(b)	Explain dual converter based DC drives.	07
Q.5	(a)	Discuss static analysis of time ratio control and current limit control.	07
-	<b>(b)</b>	Explain principle of speed control of DC motor.	07
		OR	
Q.5	(a)	Explain microcomputer control of DC drive.	07
	<b>(b)</b>	Explain operation of three phase semi converter with RLE load.	07

## \*\*\*\*\*