Enrolment No.____

Total Marks: 70

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-V- EXAMINATION – SUMMER 2016 Subject Code: 151006 Date: 17/05/2016

Subject Name: Applied Electronics (Institute Elective - II)

Time: 02:30 PM to 05:00 PM

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

Q.1	(a)	Draw and explain Block diagram and voltage transfer characteristics of an Ideal Op-amp. What is virtual ground concept?	07
	(b)	What is Ideal Voltage source? Also explain factors affecting the voltage regulation with block diagram of Shunt voltage regulator.	07
Q.2	(a)	Derive the expression of pulse width for monostable multivibrator. Design a monostable multivibrator using IC 555 for Vcc=12V and pulse width of 1msec.	07
	(b)	What is TRIAC? Draw and explain the construction of TRIAC? Also explain its operation.	07
		OR	
	(b)	Explain the working of DIAC(Diode A.C. Switch) with equivalent circuit and I-V characteristics of it.	07
Q.3	(a)	Explain the principle of Digital Storage Oscilloscope with block diagram.	07
	(b)	Explain fuzzy logic system to improve the performance of washing machine in	07
		detail.	
		OR	
Q.3	(a)	(i) Enlist differences between linear and switch mode regulator.	04
		(ii) Compare Photovoltaic Sensors with Photoconductive sensors.	03
	(b)	What is transducer? Give characteristics of transducer and explain it. Also List the factors affecting the selection of transducer and explain it.	07
Q.4	(a)	What is Digital Multi Meter? Draw and Explain the block diagram of DMM. Also state the advantages of DMM.	07
	(b)	Explain Analog to digital converter with necessary circuit diagram.	07
		OR	
Q.4	(a)	What is sequential circuit? Explain any one sequential circuit with necessary circuit diagram in detail.	07
	(b)	Explain characteristic of UJT. Discuss UJT as a Relaxation Oscillator with circuit and waveforms.	07
Q.5	(a)	What is combinational circuit? Explain any one combinational circuit with necessary circuit diagram in detail.	07
	(b)	Explain the principal and working of Thermocouple. Compare it with RTD. OR	07
Q.5	(a)	Explain architecture of 8051 with block diagram.	07
	(b)	Explain the optocoupler/Isolator in details. Also explain one application.	07
