Enrolment No.

Total Marks: 70

7

7

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER–VII EXAMINATION – SUMMER 2016 ode:170807 Date:05/05/2016

Subject Code:170807

Subject Name:Power System Analysis (Department Elective - I)

Time:02:30 PM to 05:00 PM

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- **3.** Figures to the right indicate full marks.
- Q.1 (a) Explain the significance of single phase solution of balanced 3 phase 7 network.
 - (b) Define per unit system. Derive the formulae of per unit impedance with 7 usual notations.
- **Q.2** (a) Derive the per unit model of single phase transformer .
 - (b) A 100 MVA, 11 kV generator with Xd" = 20 % is connected through a transformer, line and a transformer to a bus that supplies three identical motors as shown in Fig. 1. Each motor has Xd" = 25 % and Xd' = 30% on a base of 15 MVA, 6.6 kV. The three-phase rating of the step-up transformer is 50 MVA, 11/66 kV with a leakage reactance of 10 % and that of the step-down transformer is 50 MVA, 66/6.6 kV with a leakage reactance of 10%. The bus voltage at the motors is 6.6 kV when a three-phase fault occurs at the point F. For the specified fault, calculate
 - (a) the subtransient current in the fault,
 - (b) the subtransient current in the breaker

OR

- (b) Discuss the Symmetrical Short Circuit MVA Rating of Circuit Breaker. 7
- **Q.3** (a) State the percentage occurrence of unsymmetrical fault. What is α ? With **6** usual notations prove that $1 + \alpha + \alpha^2 = 0$.
 - (b) Briefly explain the significance of negative sequence impedance and 4 negative sequence network model of alternator for fault analysis.
 - (c) What is zero sequence network? State its role in fault analysis. Draw the zero sequence network of 3 phase star to star transformer with both winding grounded and 3 phase delta to delta transformer.

OR

- **Q.3** (a) With usual notations prove that $[Vs] = [A]^{-1} [Vp]$.
 - (b) Briefly Explain the positive sequence network for the electrical power 6 system.
- **Q.4** (a) Draw the connections of a sequence network for single line to ground **4** fault.

8

- (b) Derive the formulae for positive sequence current Ia1 when 3 phase **6** transmission line is subjected to double line to ground fault.
- (c) Draw the connection of sequence network for the following cases of open 4 conductor fault. (i) one conductor open (ii) two conductor open

OR

Q.4	(a)	State the comparisons for various methods of load flow solutions.	6
	(b)	Explain the decoupled load flow solution method .	8
Q.5	(a)	Derive the equation of per unit value of moment of inertia for the synchronous machine subjected to acceleration due to input feed of mechanical energy.	7

(b) With usual notations prove the condition for equal area criterion for a 7 machine swinging with respect to infinite bus.

OR

- **Q.5** (a) Derive the swing equation describing the rotor dynamics for synchronous **6** machines.
 - (b) A synchronous generator o f reactance1 .20 p. u. is connected to an infinite bus bar (IVI = 1.0 p.u.) through transformers and a line of total reactance o f 0.60 p.u. The generator no load voltage is 1.20 p.u. and its inertia constant is H = 10 MW/MVA.The resistance and machine damping may be assumed negligible. The system frequency is 50 Hz. Calculate the frequency of natural oscillations if the generator is loaded to (1) 60% and (ii) 80% of its maximum power limit.

7