

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VII EXAMINATION – SUMMER 2016****Subject Code:172401****Date:16/05/2016****Subject Name:Power Electronics Systems Modelling****Time:02:30 PM to 05:00 PM****Total Marks:****70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw and explain the block diagram of Power Electronics System with reference to modeling. **07**
(b) Explain in brief normalized model. **07**
- Q.2** (a) State and explain inductor volt second balance principle. **07**
(b) Draw PWM model with necessary waveforms. **07**
- OR**
- (b) Explain the manipulation of buck converter model into canonical form. **07**
- Q.3** (a) Find out the steady state output voltage for a buck chopper using small-ripple approximation. Draw necessary diagrams & waveforms. **07**
(b) Discuss the concept of nonlinearity and the importance of perturbation & linearization with respect to power electronics. **07**
- OR**
- Q.3** (a) Derive the equation for voltage conversion ratio $M(D)$ for a boost converter and draw its graph. **07**
(b) List the major steps of engineering design process. Explain each in brief. **07**
- Q.4** (a) Explain the concepts of Controllability and Observability. **07**
(b) Define the following: Model, Controllability, Observability, MIMO, Normalization, Impulse Response, Linearization **07**
- OR**
- Q.4** (a) Develop the model of a DC motor. **07**
(b) Explain the close loop speed control of DC motor using power electronics converter. **07**
- Q.5** (a) Explain the state space model of a buck converter. **07**
(b) Draw and explain the ideal and physical models of AC transformer. **07**
- OR**
- Q.5** (a) Develop the state space model of a boost converter along with necessary figures. **07**
(b) Explain the modelling of PWM inverter. **07**
