Seat No.:	Enrolment No.

Subject Name: Advanced Power Electronics II (Department Elective - II)

Subject Code:180907

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-VIII EXAMINATION - SUMMER 2016

Date:16/05/2016

	ime: struct	10:30 AM to 01:00 PM Total Marks: 70 ions:	0
		 Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. 	
Q.1	(a) (b)	Derive the equation of instantaneous power and define active and reactive power from it. Explain the Graetz circuit with necessary diagram and also obtain the expression of output voltage.	07 07
Q.2	(a) (b)	Explain load compensation and system compensation with the help of phasor diagram. State & discuss the factors to be given due care while designing the Shunt & Series compensators.	07 07
	(b)	OR Draw schematic diagram of Bipolar HVDC transmission system and explain working of each component in brief.	07
Q.3	(a)	In view of reactive power control, explain working of synchronous condensers with	07
	(b)	schematic diagram. Compare various kinds of SVC devices.	07
		OR	
Q.3	(a)	Explain the working of three-phase Thyristor Controlled Reactor (TCR) with neat	07
	(b)	diagrams. How to reduce harmonics introduced by three phase TCR? Explain different types of HVDC systems.	07
Q.4	(a)	Derive the equation for rating of series and shunt compensator. Compare rating of Series & Shunt Compensator.	07
	(b)	Explain working of 12 pulse converter with suitable circuit diagram and waveforms. State its advantages over 6-pulse converter. OR	07
Q.4	(a)	Give comparison between CSC (Classical HVDC) and HVDC-VSC systems.	07
	(b)	Explain the effect of source inductance on converter output voltage. Also obtain expression of DC output voltage with overlap angle.	07
Q.5	(a)	Discuss advantages and disadvantages of HVDC system over HVAC system.	07
	(b)	Develop the complete equivalent circuit of an HVDC link and obtain the expression for the dc current in DC link as $I_d = V_{d0r} - V_{d0i}$ / $R_{eq.}$ OR	07
Q.5	(a)	How compounding of rectifiers can be done? Explain current compounding of an inverter.	07
	(b)	Explain Inverter Extinction Angle Control.	07
