

Seat No.: \_\_\_\_\_

Enrollment No. \_\_\_\_\_

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE - SEMESTER- 1<sup>st</sup> / 2<sup>nd</sup> EXAMINATION (NEW SYLLABUS) – SUMMER 2016**

**Subject Code: 2110005**

**Date: 08/06/2016**

**Subject Name: Elements of Electrical Engineering**

**Time: 2.30 to 5.00 PM**

**Total Marks: 70**

**Instructions:**

1. Question No. 1 is compulsory. Attempt any four out of remaining Six questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- | <b>Q.1</b> | <b>Objective Questions.</b>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                               | <b>Mark</b>                         |
|------------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------------------------------------|
|            | <p><b>(a)</b></p> <ol style="list-style-type: none"><li>1. The unit of current is _____.<br/>(a) Volt/sec (b) coulomb/sec (c) amp/sec (d) none of these</li><li>2. Coulomb's second law is called as _____ law.<br/>(a) Inverse square (b) charge (c) induction</li><li>3. If the length of conductor is doubled and its cross sectional area is reduced to 50% then its resistance will be _____.<br/>(a) Same (b) doubled (c) increased by 4 times (d) reduced to 1/4th</li><li>4. A conductor carries 10A in a direction perpendicular to a magnetic field of density 0.3T. If the length of conductor is 10 cm the force on the conductor <math>F=</math> _____.<br/>(a) 3 N (b) 0.3 N (c) 30 N</li><li>5. Amount of light produced by a lamp or the amount of heat produced by an iron is proportional to the _____.<br/>(a) Square of RMS value (b) RMS value (c) square of average value (d) average value.</li><li>6. The three phase voltages are displaced by _____ radians from each other.<br/>(a) <math>\pi/2</math> (b) <math>\pi/3</math> (c) <math>2\pi/3</math> (d) <math>\pi</math></li><li>7. Define Lumens.</li></ol> | <b>07</b>                           |
|            | <p><b>(b)</b></p> <ol style="list-style-type: none"><li>1. The resistance of a thin conductor is _____ as compared to that of a thick conductor.<br/>(a) Same (b) lower (c) higher</li><li>2. The value of relative permittivity for Air is _____.</li><li>3. A magnetic circuit has mean length of 20 cm and cross sectional area of 1 cm<sup>2</sup> if the flux density is 2T then <math>\Phi=</math> _____.<br/>(a) <math>2 \times 10^{-4}</math> mWb (b) <math>2 \times 10^{-4}</math> Wb (c) <math>2 \times 10^{-2}</math> Wb (d) none of these</li><li>4. Define RMS value.</li><li>5. Draw the phasor diagram of R-C series circuit.</li><li>6. For a balanced delta load the _____ of all their line currents is zero.<br/>(a) Product (b) difference (c) sum (d) division</li><li>7. Define A-H efficiency.</li></ol>                                                                                                                                                                                                                                                                                                           | <b>07</b>                           |
| <b>Q.2</b> | <p><b>(a)</b> Explain the effect of temperature on different metals.</p> <p><b>(b)</b> Explain Current and Voltage divider rule.</p> <p><b>(c)</b> Derive expression for delta to star conversion of resistive network.</p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                               | <b>03</b><br><b>04</b><br><b>07</b> |

- Q.3** (a) Derive the expression for the equivalent capacitance of capacitors connected in parallel. **03**
- (b) The equivalent capacitance of two capacitors when connected in series is  $0.03 \mu\text{F}$  & when connected in parallel is  $0.16 \mu\text{F}$ . Find the capacitance of both the capacitors. **04**
- (c) Three capacitors having capacitances of  $10 \mu\text{F}$ ,  $20 \mu\text{F}$  and  $40 \mu\text{F}$  are connected in series to a  $400 \text{ V}$  d.c. source. Find (i) Total capacitance (ii) Total charge in circuit (iii) Total energy stored. **07**
- Q.4** (a) Explain Magnetic Hysteresis phenomena using hysteresis loop. **03**
- (b) State similarities between magnetic circuit and electrical circuit. **04**
- (c) Define co-efficient of coupling. Derive the relation between self and mutual inductance. **07**
- Q.5** (a) Three currents are represented by  $i_1 = 10\sin\omega t$ ,  $i_2 = 20\sin(\omega t - \pi/6)$ ,  $i_3 = 30\sin(\omega t + \pi/4)$ . Find magnitude and phase angle of resultant current of their addition. **03**
- (b) An inductive coil draws  $10 \text{ A}$  current and consume  $1 \text{ KW}$  power from a  $200\text{V}$ ,  $50\text{Hz}$ , Ac supply determine (1) the impedance in Cartesian and polar form (2) power factor (3) reactive and apparent power. **04**
- (c) Prove the condition of resonance for series R-L-C AC circuit. Also analyze the phenomena with the help of graph. **07**
- Q.6** (a) Give advantages of Two Wattmeter Method. **03**
- (b) For a balanced delta connected load supplied at 3-phase,  $400 \text{ V}$  ac supply, the two wattmeter readings are:  $7.8\text{kW}$  and  $-2.55\text{kW}$ . Find out load power factor & line current. **04**
- (c) Establish relation between line voltage & phase voltage and current relation in 3-phase star connection. Draw phasor diagram. **07**
- Q.7** (a) Classify various types of Lighting scheme and explain any two. **03**
- (b) State types of Fuse and explain any one. **04**
- (c) Explain construction of cable in detail. **07**

\*\*\*\*\*