Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III(New) EXAMINATION - SUMMER 2016

Subj	ect	Code:2131004 Date:27/05/2	016
Subj	ect	Name:Digital Electronics	
•		0:30 AM to 01:00 PM Total Marks	s: 70
Instru	ıctio	ns:	
	1.	Attempt all questions.	
		Make suitable assumptions wherever necessary.	
	3.	Figures to the right indicate full marks.	
Q.1		Short Questions.	14
V.1	1.	What is difference between latch and flip-flop?	
	2.	Define Fan-out.	
	3.	What is the use of state diagram?	
	4.	Which gates are called as universal gates? What are its advantages?	
	5.	State the associative property of Boolean algebra	
	6.	List the types of ROM.	
	7.	What are called Don't care conditions?	
	8.	What is propagation delay?	
	9.	What is prime implicant?	
	10.	· · · · · · · · · · · · · · · · · · ·	
	11.		
		Which TTL logic gate is used for wired ANDing?	
	13. 14.	What is a state equation? Define Nibble.	
	14.	Define Nibble.	
Q.2	(a)	Explain the working of multiplexer.	3
	(b)		4
	(c)	1	7
		OR	
	(c)	Write short note on half adder and full adder.	7
0.1	(.)	Define the fellowing towns	2
Q.3	(a)	<u> </u>	3
	(b)		4
	(D)	them.	7
	(c)		7
	(0)	OR	•
Q.3	(a)		3
•	` ′	I. Given that $(16)_{10} = (100)_x$, find the value of x.	
		II. Add (6E) ₁₆ and (C5) ₁₆	
		III. $(4433)_5 = ()_{10} = ()_2$	
	(b)		4
		I. $(1011011101101110)_2 = ($ $)_{16}$	
		II. Subtract (45) ₈ from (66) ₈	
		III. Covert the Gray code 1101 to binary	
		IV. Find the XS-3 code of 37	_
	(c)		7
		corresponding logic diagrams.	

Q.4	(a)	Give the applications of Decoder.	3
	(b)	Implement the given function using multiplexer $F(A,B,C) = \Sigma m(1,2,4,7)$	4
	(c)	Reduce the expression $F = \Sigma m(0,2,3,4,5,6)$ using K-map and implement using NAND gates only.	7
		OR	
Q.4	(a)	Reduce the expression $F = ((AB)^2 + A^2 + AB)^2$	3
	(b)	Explain the types of finite state machines?	4
	(c)	Distinguish between combinational and sequential logic circuits. Give the applications of flip-flops.	7
Q.5 ((a)	Write a short note on FPGA.	3
	(b)	Design 4-to-16 Decoder from two 3-to-8 Decoders.	4
	(c)	Design a synchronous BCD counter with JK flip-flops.	7
		OR	
Q.5	(a)	Implement T flip flop using D flip flop.	3
	(b)	Give the comparison between synchronous and asynchronous counters.	4
	(c)	Write a note on Memory.	7
