Seat No.:	Enrolment No.

Subject Code:2140305

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER-IV(New) EXAMINATION - SUMMER 2016** 

Date:01/06/2016

Subject	Nan	ne:Analog Circuits-II	
•			Total Marks: 70
Instruction	ns:		
		empt all questions.	
	2. Make suitable assumptions wherever necessary.		
3.	Figu	res to the right indicate full marks.	MADEC
			MARKS
Q.1		Short Questions	14
	1	What is the need of Isolation amplifier?	
	2	What is the difference between Instrumentation ampl	ifier
		and differential amplifier?	
	3	Define Quality factor Q for filter.	
	4	What is the meaning of noise corner frequency?	
	5	What is the need of all pass filter design?	
	6	Define Noise floor.	
	7	What is the need of modulation?	
	8	Explain functionality of Frequency analyzer.	
	9	What is Mutual capacitance?	
	10	$\mathcal{E}$	
	11		veen
	12	two circuits.	<del>f</del> aaa
	12	How twisted pair cables minimize the inductive interbetween them?	Tace
	12		
	_	Define Burst Noise.	
	14	Enlist the component of CRO tube.	
Q.2	<b>(a)</b>	What is thermal noise? How it will affect the working	ng of <b>03</b>
		analog circuit?	
	<b>(b)</b>	· · · · · · · · · · · · · · · · · · ·	04
	<b>(c)</b>	Give the design of Instrumentation amplifier and de	erive 07
		its gain equation.	
		OR	07
0.2	(c)	Explain Op-amp noise circuit model.	07
Q.3	(a)		03 encv 04
	<b>(b)</b>	Explain the concept of noise colors with their frequencement.	ency <b>04</b>
	(c)	Explain the fundamental of Low pass filter. What is	s the <b>07</b>
	(C)	effect of order on filter response?	s the <b>U</b> 7
		OR	
Q.3	(a)	<u></u>	ation 03
V.2	(a)	amplifiers.	UJ
	<b>(b)</b>	Discuss technical aspects of AM Transmitter	and <b>04</b>
	(~)	receiver.	
	(c)	Discuss the design aspects of First order noninver	rting <b>07</b>
	` /	configuration of Low pass filter.	<i>C</i> -

<b>Q.4</b>	(a)	Explain design of Chopper stabilized amplifier.	
	<b>(b)</b>	Compare CRO and DSO.	04
	(c)	Explain design aspects of General Sallen-Key High-Pass Filter.	07
		OR	
Q.4	(a)	Design a second order Low pass filter at a high cutoff frequency of 1 KHz.	03
	<b>(b)</b>	Discuss the FM demodulation techniques.	04
	(c)	Explain design aspects of Sallen-Key Band-Pass filter.	07
· · · ·		Explain schematic of Single point and multipoint ground techniques.	03
	<b>(b)</b>	Discuss available Safety Standards In Medical Electronic Amplifiers.	04
	<b>(c)</b>	Explain techniques for power supply noise reduction.	<b>07</b>
		OR	
Q.5	(a)	Explain the various methods of noise coupling.	03
	<b>(b)</b>	Explain Electrostatic discharge (ESD) protection techniques with necessary schematic.	04
	<b>(c)</b>	How shielding can affect the capacitive coupling?	<b>07</b>

\*\*\*\*\*