Enrol	lment	No	
	mont	110.	

## GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-IV(New) EXAMINATION – SUMMER 2016

	Subject Code:2141706 Date:06/06/2		16
	Tim	Subject Name:Analog Signal Processing Time:10:30 AM to 01:00 PM Total Marks: Instructions:	
	msur	<ol> <li>Attempt all questions.</li> <li>Make suitable assumptions wherever necessary.</li> <li>Figures to the right indicate full marks.</li> </ol>	
			MARKS
Q.1	1 2 3	Short Questions Define CMRR. Which type of feedback is used in inverting op-amp? What is the purpose of differential amplifier stage in internal circuit of Op-	14
	4 5 6	What is the basic difference between comparator and Schmitt Trigger circuit? What is the name of the circuit that is used to detect the peak Value of non-sinusoidal input waveform? What are the two requirements for oscillation?	
	7 8 9 10 11	What is VCO? Define slew rate. What is the offset-minimizing resistor R <sub>OM</sub> ? In op-amp if (+) terminal is grounded (-) terminal also acts as ground. Why? The voltage required to force the differential output to zero is called	
	12	Calculate the cutoff frequency of a first-order low-pass filter for $R1=2.5k\Omega$ and $C1=0.05\mu$ F	
Q.2	13 14 (a) (b)	What is the voltage gain of voltage follower circuit? Input impedance of the ideal operational amplifier is Explain Positive clipper with necessary waveform for +Vref and -Vref. Derive exact expressions for voltage gain of inverting amplifier. Also explain	03 04
	(c)	its application as an inverter. Explain Instrumentation amplifier and derive formula for voltage gain. <b>OR</b>	07
	(c)	Draw op-amp based full wave rectifier (absolute-value output) circuit. Explain its working with necessary input/output waveforms.	07
Q.3	(a) (b) (c)	Explain positive small signal half wave rectifier circuit. Design first order High pass filter at a cut-off frequency of 1KHz with a passband gain of 2. Assume C=0.01µf. Explain operation of Binary weighted resistor type DAC. Enlist advantages &	03 04 07
		disadvantages. OR	
Q.3	(a)	Draw an op-amp based differential amplifier circuit and obtain expression for its differential gain.	03
Q.4	(b) (c) (a)	Explain wide band-pass filter with necessary diagrams. What is ADC? Explain SAR type ADC. Explain Logarithmic amplifier with its circuit diagram.	04 07 03
	(b) (c)	What is $I_B$ ? What is cause of $I_B$ ? Explain technique to reduce effect of offset voltage due to $I_B$ . Explain Timer IC 555 as Astable multivibrator. Enlist application and explain any one in detail.	04 07
		•	1

## OR

Q.4	<b>(a)</b>	Explain summing amplifier using non- inverting configuration of op-amp.	03
	<b>(b)</b>	Draw AC amplifiers with a single supply voltage. also draw input output waveforms.	04
	(c)	Explain block diagram of IC 555 timer.	07
Q.5	<b>(a)</b>	Explain voltage to current converter with floating load.	03
	<b>(b)</b>	Sketch op-amp based basic integrator circuit. Derive expression for output voltage to justify its operation of integration.	04
	(c)	Explain RC Phase shift (Constant frequency low audio frequency) oscillator with necessary waveforms. Enlist advantages, disadvantages and applications it.	07
		OR	
Q.5	<b>(a)</b>	Explain voltage follower and its application.	03
-	<b>(b)</b>	Explain how op-amp can be used as a differentiator.	04
	(c)	Explain working of op-amp based Schmitt trigger circuit along with schematic and input/output waveforms.	07

\*\*\*\*\*