GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER- 1st / 2nd EXAMINATION- SUMMER 2016

Subject Code: TEE011

Date:15/06/2016

Subject Name: Basic Electronics Time:02:30 PM to 5:00 PM


Total Marks: 70

07

Instructions:

Seat No.: ___

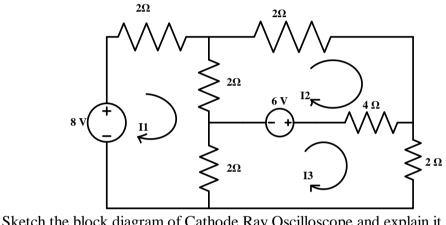- 1. Attempt any five questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Classify the electrical energy sources and explain in brief. 07
 - (b) Explain Resisters, Capacitors and Inductors in brief.
- **Q.2** (a) Determine the Current through 4 Ω resistor branch of the following network 07 using Mesh analysis.



	(b)	Sketch the block diagram of Cathode Ray Oscilloscope and explain it.	07
Q.3	(a)	Explain the superposition theorem to solve the multisource network with example.	07
	(b)	Explain the Norton's theorem to solve the network with example.	07
Q.4	(a)	Explain the DELTA-WYE transformation in brief with necessary equations and circuit diagrams.	07
	(b)	Explain the KCL and KVL with equations.	07
Q.5	(a) (b)	Draw the amplifier block and write down the characteristics of ideal Op-amp. Draw and explain the circuit diagram of Inverting and Non-inverting amplifier using Op-amp.	07 07
Q.6	(a)	Draw and explain the circuit diagram of adder and integrator circuits using Op- amp.	07
	(b)	Sketch the block diagram of Computer systems and explain each block.	07
Q.7	(a) (b)	Draw and explain different network topologies. Draw the symbols and write down the truth tables of two input AND, OR, NOT, NAND, NOR, EX-OR, EX-NOR gates.	07 07
