Seat No.:	Enrolment No

Subject Code: 141101

## GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-IV EXAMINATION – WINTER 2015

Date:30/12/2015

•	e: 02	Jame: Advance Electronics 30pm to 05:00pm Total Marks: 70	
insti u	1. 2. 1	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	Explain the parameters those affecting to the transistor at high frequencies. Draw the hybrid $\pi$ model for CE configuration and also explain why we cannot use the h-parameters for the analysis at high frequencies.	07
	<b>(b)</b>	Explain Cascaded Amplifier and also Derive the expression for the overall gain in decibels of an n-stage cascaded amplifier and why to express gain in dB?	07
Q.2	(a)	Compare different types of power amplifier based on conduction angle, position of Q-point, efficiency and distortion.	07
	<b>(b)</b>	Explain the single stage CE transistor amplifier response. Derive the expression for transfer function for exact analysis.  OR	07
	<b>(b)</b>	What is feedback? List the advantages of negative feedback. Derive relation between gain with and without feedback in a transistor amplifier.	07
Q.3	(a) (b)	Explain Clapp Oscillator using transistor and FET. Design a Hartley oscillator using BJT for an output frequency of 50 KHz. Assume $V_E=3V$ , $V_{CEQ}=3V$ , $V_{CC}=10V$ , $I_{CQ}=1mA$ , $\beta=50$ & $C=0.01\mu f$ OR	07 07
Q.3	(a) (b)	State and explain any seven characteristics of an ideal Op-Amp. Explain the Features of IC 741 and Pin Configuration with diagram.	07 07
Q.4	(a)	Explain Voltage series, Voltage shunt, Current series and Current shunt Feedbacks in brief.	07
	<b>(b)</b>	What is an Oscillator? Explain the concept of oscillator. Explain the concept of oscillator properly with Barkhausen Criteria.  OR	07
Q.4	(a) (b)	Explain the analysis of Dual Input and Balanced Output Differential Amplifier.  Define the Following Terms:  (1)Slew rate (2)PSRR (3)Fan-in and Fan-out (4)Noise immunity  (5) Propagation Delay (6)Figure of merit (7)Gain bandwidth product	07 07
Q.5	(a) (b)	List the logic family. Give Comparison of each of them. Explain Dual slope A/D converter.	07 07
Q.5	(a)	<b>OR</b> What is Digital to Analog Convertor? Draw and Explain R-2R DAC? Also give the advantages and disadvantages of R-2R Digital to Analog convertor.	07
	<b>(b)</b>	Explain Resistor Transistor Logic and Direct Coupled Transistor Logic with advantages and disadvantages	07

\*\*\*\*\*