## GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-V EXAMINATION – WINTER 2015

Subject Code: 150203Date:08/12/2015Subject Name: Power Electronics and Control EngineeringTime: 10:30am to 1:00pmTotal Marks: 70Instructions:1. Attempt all questions.2. Make suitable assumptions wherever necessary.3. Figures to the right indicate full marks.			
Q.1	(a) (b)	State & explain various methods to turn on SCR. Explain the construction and characteristics of the TRIAC.	07 07
Q.2	<b>(a)</b>	Explain following instructions with example.	07
	(b)	(i) STA (ii) ORA (iii) ADD (iv) LXI (v) LDAX (vi) RLC (vii) MVI Draw & explain torque-speed characteristics of DC motor. <b>OR</b>	07
	<b>(b</b> )	Explain leading & trailing tube circuits.	07
Q.3	(a) (b)	Explain speed control of DC motor using SCRs. Explain construction & characteristics of UJT with neat diagram. <b>OR</b>	07 07
Q.3	(a) (b)	Explain resistance welding system with necessary diagram. Explain V-I characteristics of 3-phase Induction motor.	07 07
Q.4	<b>(a)</b>	Explain the basic principle of operation of induction heating and list the advantages of induction heating.	07
	<b>(b</b> )	Draw the pin diagram of microprocessor 8085.	07
Q.4	(a)	<b>OR</b> Explain the operation of dielectric heating and its high frequency power supply for dielectric heating.	07
	<b>(b</b> )	Explain the programming registers model and flag register in detail.	07
Q.5	<b>(a)</b>	What is Analog to digital converters? Explain successive-approximation type	07
	(b)	A/D converter in detail with its advantages. Explain thermocouple in brief. <b>OR</b>	07
Q.5	(a) (b)	Draw the block diagram of PLC and describe each block in detail. Draw the circuit diagram of ignitron contactor & explain its working. Where it is used?	07 07

## \*\*\*\*\*