GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-V EXAMINATION – WINTER 2015

Subject Code: 151003Date:17/12/2015Subject Name: Integrated Circuits and ApplicationsTotal Marks: 70Instructions:Total Marks: 70


- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Explain the use of differential amplifier using three op-amps as instrumentation 07 amplifier
 - (b) Define the terms: Slew rate, CMRR, input bias current and output offset voltage. 07
- Q.2 (a) Explain working of op-amp based Schmitt trigger circuit along with 07 Schematic and input/output waveforms.
 - (b) Draw & explain the basic integrator circuit. What are the problems with it? 07 Modify the circuit to obtain practical integrator & prove that it solves the problem of basic integrator circuit.

OR

- (b) Draw & explain the basic differentiator circuit. What are the problems associated with it? Modify the circuit to obtain practical differentiator & prove that it solves the problem of basic differentiator circuit.
- Q.3 (a) Explain the following application of op-amp (1) Small signal Half wave rectifier 07 (2) Peak Detector
 - (b) Draw basic log amplifier using a transistor. Derive the expression for output 07 voltage

OR

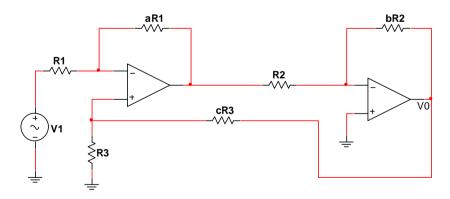Q.3(a) Explain the application of op-amp as a positive and negative clipper circuit.07(b) Prove that V0/V1=a*b/1+b[((1+a)/(1+c)])07



- Q.4 (a) Design and explain first order low pass Butterworth filter at cut-off frequency of 1 KHz with pass band gain of 2.Draw circuit with component value.
 - (b) Classify filters with four basic types. Explain ideal and practical characteristics of **07** all. Draw attenuation characteristics also.

OR

Q.4 (a) Discuss magnitude and frequency scaling in filter design.

1

- (b) Sketch Delyiannis-Friend circuit and obtain its transfer function.
- Q.5 (a) Explain working of 555 timer based monostable multivibrator. Design the same 07 for the output pulse width of 10 ms.
 - (b) What are the different types of voltage regulators? Discuss LM317 based 07 adjustable voltage regulator. Indicate bypass capacitors to improve transient response and protective diodes in the connection diagram.

OR

- **Q.5** (a) What is PLL? Explain operation of PLL with basic blocks.
 - (b) State the applications of operational transconductance amplifier and explain any 07 one with necessary circuit and derivation

07

07