Seat	No.:	

Enrolment No._____

GUJARAT TECHNOLOGICAL UNIVERSITY **BE – SEMESTER – VI EXAMINATION – WINTER 2015** Subject Code:160801 Date:15/12/ 2015 Subject Name: Integrated Circuit & Application **Time:2:30pm to 5:00pm Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. Q-1 What is op-amp? Draw and explain the block diagram representation of a typical 07 **(A)** Op-amp. Explain absolute value output circuit. 07 **(B)** Q-2 **(A)** Define thermal drift and error voltage. Derive equation of error voltage. 07 **(B)** Explain the peaking amplifier. 07 OR Explain Differential input Differential output amplifier. 07 **(B)** Q-3 What is an instrumentation amplifier? Explain it with suitable example. 07 **(A)** 1) Explain the ideal voltage transfer curve. 04 **(B)** 2) Explain the equivalent circuit of practical op-amp. 03 OR Explain the difference between bandwidth, transient response and slew rate. 0-3 07 **(A)** Explain the practical integrator circuit. Explain its advantages. Also draw its **(B)** 07 Frequency response. **O-4 (A)** What is slew rate? Derive the expression of it's for op-amp. 07 **(B)** Define astable, monostable, and bistable multivibrator. 07 OR 07 **Q-04 (A)** Explain Phase Locked Loop & It's application. **(B)** In an inverting adder circuit the input voltages are 0.5v, 0.3v, 0.1v while R1=R2 07 =R3=1 k Ω . if Rf=10k Ω , calculate the output voltage. Q-05 Why op-amp is generally not used in open-loop mode? Explain closed loop 07 **(A)** Configuration of op-amp. And give advantage of negative feedback. **(B)** Explain voltage to current converter with floating load with one application. 07 OR Q-05 **(A)** An Op-Amp having the following parameters is connected as a non inverting 07 amplifier with R1=1 k Ω and RF=10 k Ω : And A=200,000, Ri= 2 M Ω , Ro=75 Ω , fo= 5Hz, supply voltage= ± 15 V, output voltage swing = ± 13 v Compute the values of AF, RIF, ROF, FF, and VOOT.

(B) Write a Short note on very high input impedance circuit.

07