| Enro | lment | No. |
|------|-------|-----|
| | | |

GUJARAT TECHNOLOGICAL UNIVERSITY BE – SEMESTER – VI EXAMINATION – WINTER 2015

| Sul Tin | oject | Code:160902Date:17/12/2015Name: POWER ELECTRONICS-II30pm to 5:00pmas:Total Marks: 70 | | | |
|------------|--------------|--|----------|--|--|
| | | Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. | | | |
| Q.1 | (a) | Explain series single phase inverter with ckt. diagram and wave-form. What are the merits and demerits of it? | 07 07 | | |
| Q.2 | (b) (a) | Give comparison between series and parallel inverter. Explain half-bridge topology with resistive load. | | | |
| | (b) | Derive Fourier Analysis of load voltage wave-form of Half wave Inverter topology. | 07 | | |
| | | OR | | | |
| | (b) | Explain 120 degree mode of three phase bridge inverter with star connected resistive load. | 07 | | |
| Q.3 | (a) | Explain 180 degree mode of operation for three phase bridge inverter with resistive load. | 07 | | |
| | (b) | Explain Sine wave PWM technique. What is the effect of modulation index on output? Explain its merit and demerit. | 07 | | |
| Q.3 | (a) | OR Explain Harmonic and Total harmonic distortion factor for inverter. | 07 | | |
| | (b) | What is the third harmonic injection method for PWM techniques? What are merits of it over sine wave PWM? | 07 | | |
| Q.4 | (a) | Explain basics of single phase current source inverter with circuit diagram. | 07 | | |
| | (b) | Explain principle of integral cycle control for AC voltage controller. | 07 | | |
| | OR | | | | |
| Q.4 | (a) | Explain single phase full-wave AC controller with circuit diagram and wave form. | 07 | | |
| | (b) | Explain working of Matrix AC to AC converter. | 07 | | |
| Q.5 | (a) | Explain constant V/F control with the help of block diagram for Induction motor. | 07 | | |
| | (b) | Explain rotor resistive control for induction motor using power electronics device. | 07 | | |
| | | OR | | | |
| Q.5 | (a) (b) | What are the merits of HVDC? Explain working of HVDC with regards to power electronics. Explain working of Electronic Ballast? How power electronics play role in it? | 07 07 | | |
| | (0) | What are the merits of it over choke ballast? | | | |