Seat No.: Enrolment No.

Subject Code:160905

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER - VI EXAMINATION - WINTER 2015

Date:10/12/ 2015

Ti	me:2 structi 1 2	t Name: Electrical and Electronic Measurement 2:30pm to 5:00pm Total Marks: 70 ons: Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	Define the following terms Gaussian distribution of data (1) Precision index (2) Probable error (3)Standard deviation of mean (4) Standard deviation of Standard deviation	07
	(b)	Define the term self inductance, Explain Maxwell's bridge for measurement of self inductance with vector diagram	07
Q.2	(a) (b)	State common examples of high resistance measurements; explain difficulties in measurement of high resistances. Describe Kelvin's double Bridge with neat diagram	07
	(6)		0.
	(b)	A Wheatstone bridge has ratio arms of 1000 Ω and 100 Ω and being used to measure an unknown resistance of 25 Ω . Two galvanometers are available. Galvanometer 'A' has a resistance of 50 Ω and a sensitivity of 200 mm/ μ A and Galvanometer 'B' has a resistance of 600 Ω and a sensitivity of 500 mm/ μ A. Which of the two galvanometer more in sensitivities? Comment upon the results.	07
Q.3	(a) (b)	Describe sources and null detectors used in a.c. bridge. What are the errors in the measurement of A. C. bridge? Suggest remedies for eliminating errors.	07 07
Q.3	(a)	OR How can the frequency be determined using a bridge? Draw this bridge and derive condition for balance. Why and how two resistances and capacitances are made	07
	(b)	equal? Explain Schering Bridge with diagram.	07
Q.4	(a)	Why instrument transformer is required? justify the statement "Never open secondary winding circuit of a current transformer while its primary winding is energized"	07
	(b)	Explain Heterodyne wave analyzer.	07
Q.4	(a)	OR A C.T has a single turn primary and a 200 turns secondary winding. A secondary winding supplies a current of 5 A to a non-inductive burden of 1 Ohm. The requisite flux is set up in the core by mmf of 80Amp . The frequency is 50 Hz and the net cross section of the core is $1000~\text{mm}^2$. Calculate the ratio and phase angle of the transformer .Also find flux density in the core. Neglect all losses .	07
	(b)	Explain harmonic distortion analyzer	0′

Q.5	(a)	Discuss the Varley loop test method for detection of cable fault.	07
	(b)	Describe the method for determination of B-H curve of magnetic material.	07
		OR	
Q.5	(a)	Explain Murray loop test for location cable fault	07
	(b)	Explain method for measurement of flux density	07
