Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-VII EXAMINATION – WINTER 2015


Subject Code: 170807 **Subject Name: Power System Analysis Time: 10:30am to 1:00pm**

Date: 04/12/2015


Total Marks: 70

- **Instructions:**
 - 1. Attempt all questions.
 - 2. Make suitable assumptions wherever necessary.
 - 3. Figures to the right indicate full marks.
- Q.1 (a) Prove that per unit impedance of transformer is the same whether computed 07 from primary or secondary side. Draw per unit equivalent circuit of single-phase transformer.
 - (b) Prepare per unit impedance diagram for the power system as shown in figure. 07 Choose a base of 100 MVA, 22 kV on the generator side. The three phase load at bus 4 absorbs 60 MVA, 0.6 p.f. lagging at 10.5 kV. Line 1 and line 2 have a reactance of 50 Ω and 65 Ω respectively. The rating of generator, motor and transformers are:

G:	100 MVA	22 kV	X= 0.18 p.u.
T ₁ :	50 MVA	22/220 kV	X=0.1 p.u.
T ₂ :	40 MVA	220/11 kV	X=0.06 p.u.
T ₃ :	40 MVA	220/110 kV	X=0.065 p.u
T ₄ :	50 MVA	110/11 kV	X=0.08 p.u.
M:	70 MVA	11 kV	X= 0.2 p.u

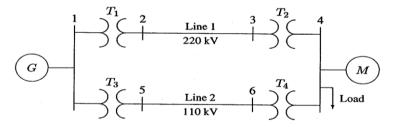

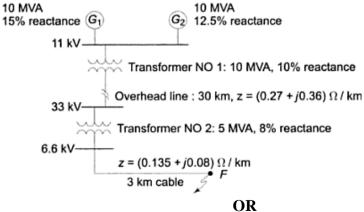- (a) Draw the waveforms for fault current for a 3-phase fault on alternator terminals. 07 **O.2** Explain the sub-transient, transient and steady state reactance. What is their significance in fault calculations?
 - (b) For the radial network shown in fig., a three phase fault occurs at F. Determine 07 the fault current and the line voltage at 11 kV bus under fault condition.



- (b) Derive fault current equation $I^f = V_r^0/(Z_{rr} + Z^f)$ Using Z_{bus} Matrix when n bus **07** system is given. (assume that the rth bus is faulted)
- Q.3 (a) Derive expression for sequence impedances of transmission line and draw their 07 sequence networks.
 - (b) Explain Zero Sequence Networks of Transformers showing various 07 connections.

OR

- Q.3 (a) Explain double line-to-ground fault. Derive expression of fault current and draw 07 the connection of sequence networks.
 - (b) Three 6.6 kV, 3-phase, 10 MVA alternators are connected to a common bus. 07 Each alternator has a positive sequence reactance of 0.15 pu. The negative and zero sequence reactance are 75% and 30% of positive sequence reactance. A single line to ground fault occurs on the bus. Find the fault current if (1) all the alternator neutrals are solidly grounded (2) one alternator neutral is grounded through 0.3 Ω resistance and the other two neutrals are isolated.
- Q.4 (a) Explain the concept of Equal Area Criterion. Draw diagrams to illustrate its application when there is a sudden short circuit on one of the parallel lines feeding an infinite bus and the fault is very close to the sending end bus.
 - (b) What do you mean by economic loading of alternators? Write the necessary 07 conditions for economic loading of alternator.

OR

- Q.4 (a) Explain and draw the flow chart for a load flow study on a power system having 07 only P-Q buses using Gauss Seidel Method.
 - (b) Explain the procedure of formulation of Y_{BUS} using singular transformation. 07 Derive the necessary equations.
- Q.5 (a) Describe the traditional technique and new approaches for improvement of 07 transient stability limit of a power system.
 - (b) A 50 Hz, 4 pole turbo- generator rated at 20 MVA and 13.2 kV has an inertia 07 constant of 9 KW-sec/kVA.
 - (i) Find the kinetic energy stored by the rotor at synchronous speed.
 - (ii) If the input power less rotational loss is 20 MW and output power is 15MW, find the acceleration in degrees per sec² and in r.p.m. per sec

OR

- Q.5 (a) Explain the effect of increasing the torque of prime mover of one of the 07 alternator.
 - (b) A 3000 -kVA ,6 pole alternator runs at 1000 r.p.m. in parallel with other machines on 3,300 –V bus bars .The synchronous reactance is 25%.Calculate the synchronizing power for one mechanical degree of displacement and the corresponding synchronizing torque.
