Seat No.: Enrolment No

Subject Code: 172401

GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-VII EXAMINATION - WINTER 2015

Date:12/12/2015

	Subject Name: Power Electronics Systems Modelling Time: 10:30am to 1:00pm Instructions: 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks.		
Q.1	(a)	What is modeling? Explain its importance and draw the block diagram of Power	08
	(b)	Electronics System with reference to modeling. What is the requirement of normalization? Explain normalization w.r.t. Frequency.	06
Q.2	(a) (b)	Explain: Controllability, Observability and normalized model. State inductor volt-second balance principle and explain its use in buck converter.	07 07
	/L\	OR	07
	(b)	State capacitor charge balance principle and explain its use in buck converter.	07
Q.3	(a)	Discuss the objectives of AC modeling and the concept of non-linearity introduced due to switching.	07
	(b)	Explain the graphical construction of series impedances using a series R-C network.	07
		OR	
Q.3	(a)	List and explain the major steps of engineering design process. What do you mean by small signal approximation? Explain with appropriate example.	07
	(b)	List and explain the different types of modeling methods with a suitable example.	07
Q.4	(a)	Develop the state space model of a boost converter with necessary equations and figures.	07
	(b)	Explain the difference between ideal and physical models of AC transformer using neat diagrams.	07
		OR	
Q. 4	(a)	Develop the model of inverter with transformer along with necessary figures and equations.	07
	(b)	Develop the state space model of a buck converter with necessary equations and figures.	07
Q.5	(a)	Explain the state space model of DC motor.	07
	(b)	Explain Canonical Circuit Model based on physical arguments giving its importance.	07
		OR	
Q.5	(a) (b)	What is circuit averaging? Discuss the steps of circuit averaging. Explain the state space model of a full bridge inverter with RL load.	07 07
