**Subject Code: 172402** 

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER-VII EXAMINATION – WINTER 2015** 

Date: 07/12/2015

Subject Name: Industrial Drives & Control - II Time: 10:30am to 1:00pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. **Q.1** (a) Discuss on modelling of Induction Machine. 07 **(b)** Discuss on vector control of Induction Motor drive. 07 Discuss on Induction Motor speed control by variation of stator voltage. **07** 0.2 (b) Draw and explain various connections for stator voltage control of 3-phase 07 Induction Motor. OR (b) Draw and explain closed loop system for Induction Motor speed control by 07 stator voltage control method. Draw and explain the thyristor configuration for a stator voltage controlled (a) 07 0.3 reversible-speed Induction Motor Drive. Also draw the speed-torque characteristics for a reversible induction motor drive. The most versatile and reliable variable-speed drive consists of a cage-rotor 07 Induction Motor which is speed controlled by variation of the stator frequency. Explain variable-frequency operation of Induction Motor. Also draw torque characteristics for this motor at constant volts / Hz. Explain the concept of sensor less control of Induction Motor Drive. 07 Q.3 (b) Discuss on parameter sensitivity and compensation of vector controlled 07 Induction Motor. Discuss on constant current operation of stator frequency controlled IM. **07** 0.4 Discuss on closed-loop operation of stator frequency controlled Induction 07 Motor. Also explain its control techniques. **Q.4** Discuss on Permanent Magnet AC Motor Drive. 07 Discuss on speed control of synchronous motor by vector control method. 07 Draw the block diagram of controlled-slip Induction Motor Drive and explain 07 Q.5(a) its operation. 07 (b) Discuss on constant-torque constant-horsepower operation of variable frequency operated IM. Also draw the typical torque-speed characteristics for such an operation. OR **Q.5** Draw & explain the schematic diagram of IM speed control by static variation 07 of external rotor resistance. Also discuss on specific field of applications of such a drive. (b) Explain the sub-synchronous static converter operation of IM under slip-power 07 recovery scheme. Also draw open-loop torque-speed characteristics for the IM of such type of operation.

\*\*\*\*\*