GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-VIII EXAMINATION – WINTER 2015

		t Code:180304 Date:12/12/201 t Name: Electronic System Design	Date:12/12/2015	
			Aarks: 70	
 Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. 				
Q.1	(a) (b)	Explain forward & reverse characteristics of Thyristor with neat diagram. Enlist & explain different turn on methods of Thyristor.	07 07	
Q.2	(a)	Draw symbols & VI characteristics of DIAC, TRIAC, LASCR, n-channel MOSFET.	07	
	(b)	Write a short note on IGBT.	07	
	(b)	OR What is commutation? Explain class D commutation technique.	07	
Q.3	(a) (b)	Explain principle & working of Stepper motor. Explain the principle of Electromechanical energy conservation. OR	07 07	
Q.3	(a) (b)	Explain construction & working of Servo motor. Give the difference between Electromagnetic and Solid state relay.	07 07	
Q.4	(a) (b)	Write a short note on Power diodes. Explain Series & Parallel Resonant Inverter. OR	07 07	
Q.4	(a) (b)	Explain different performance parameters of Rectifier. Explain Principal of Operation of Pulse Width Modulated Inverters.	07 07	
Q.5	(a) (b)	Give the principle of Step up and Step down converter. Explain Electromagnetic compatibility & Electromagnetic Interference in analog circuit.	07 07	
Q.5	(a) (b)	OR Write a short note on Buck-Boost Regulators. Briefly explain Grounding & Shielding in analog circuit.	07 07	
