## **GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-VIII EXAMINATION – WINTER 2015**

## Subject Code:180907 Subject Name: Advanced Power Electronics-II **Time: 2:30pm to 5:00pm**

## Date:12/12/2015

**Total Marks: 70** 

**Instructions:** 

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

Q.1	(a)	Derive equation showing effect of series compensation on power transfer capability of transmission line. State advantages and limitations of series compensation over shunt compensation.	07
	( <b>b</b> )	Discuss the Merits and demerits of the HVDC transmission line over HVAC transmission line.	07
Q.2	<b>(a)</b>	Explain load compensation and system compensation with the help of phasor diagram.	07
	<b>(b</b> )	Give brief comparison of different SVCs.	07
	(b)	With necessary assumptions derive the DC output voltage equation for 6-pulse line commutated converter. Also prove that displacement factor of converter is proportional to cosine of firing angle ( $\cos \Phi = \cos \alpha$ ).	07
Q.3	(a) (b)	Explain working of TCR. Derive the expression for susceptance of TCR. State & discuss the factors to be given due care while designing the Shunt & Series compensators.	07 07
0.0		OR	
Q.3	( <b>a</b> )	Give the schematic diagram of the 12-pulse converter. State its advantages over 6-pulse converter.	07
	<b>(b</b> )	Explain the working of TSC-TCR.	07
Q.4	<b>(a)</b>	Compare Mechanically switched capacitor (MSC) with Thyristor switched capacitor (TSC).	07
	(b)	Draw the typical HVDC transmission scheme and explain the equipments required for HVDC system.	07
		OR	
Q.4	(a) (b)	Discuss inverter extinction angle control (EAG) in brief. Derive the equation of reactive power and discuss why it is necessary to have reactive power compensation.	07 07
Q.5	(a) (b)	Explain Thyristor Controlled Transformer (TCT) compensator. Discuss advantages of FACTS devices. <b>OR</b>	07 07
Q.5	(a) (b)	Explain the characteristics of FC-TCR with and without coupling transformer. Draw the equivalent circuit HVDC transmission system with necessary equations and also discuss its operating characteristics in brief.	07 07

\*\*\*\*