

Seat No.: \_\_\_\_\_

Enrolment No. \_\_\_\_\_

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE - SEMESTER-1<sup>st</sup> / 2<sup>nd</sup> (NEW) EXAMINATION – WINTER 2015**

**Subject Code: 2110005**

**Date: 02/01/2016**

**Subject Name: Elements of Electrical Engineering**

**Time: 10:30am to 01:00pm**

**Total Marks: 70**

**Instructions:**

1. Question No. 1 is compulsory. Attempt any four out of remaining Six questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- |            |  |              |
|------------|--|--------------|
| <b>Q.1</b> | <b>Objective Question – select only one option out of four (MCQ)</b>   | <b>MARKS</b> |
|            | <b>(a)</b>   | <b>07</b>    |
|            | 1. Which of the following material has nearly zero temperature co-efficient of resistance ?<br>[a] Carbon                      [b] copper                      [c] porcelain                      [d] manganin   |              |
|            | 2. The unit of absolute permittivity of a medium is<br>[a] farad/coulomb                      [b] newton-m                      [c] farad/m                      [d] joule/coulomb   |              |
|            | 3. The unit of resistivity is<br>[a] Ohm / m                      [b] Ohm-m                      [c] mho/m                      [d] mho-m  |              |
|            | 4. Time constant of an R-C ckt. may be defined as<br>[a] time during which capacitor voltage rises to 0.632 of its initial value<br>[b] time during which charging current falls to 0.37 of its initial max. value<br>[c] time during which capacitor voltage falls to 0.632 of its final steady value<br>[d] time during which charging current rises to 0.37 of its initial max. value |              |
|            | 5. The unit of reluctance is<br>[a] AT / Wb                      [b] Wb / AT                      [c] 1/Henry                      [d] either [b] or [c]   |              |
|            | 6. Wh efficiency of lead-acid cell is _____ Ah efficiency.<br>[a] greater than                      [b] smaller than                      [c] equal to                      [d] none of this   |              |
|            | 7. The value of form factor is<br>[a] 11.1                      [b] 1.11                      [c] 1.414                      [d] 14.14   |              |
|            | <b>(b)</b>   | <b>07</b>    |
|            | 1. The value of power factor is zero for<br>[a] purely inductive ckt.                      [b] purely resistive ckt.<br>[c] purely capacitive ckt.                      [d] either [a] or [c]  |              |
|            | 2. For a series resonance condition of AC circuit impedance is<br>[a] minimum                      [b] maximum                      [c] zero                      [d] infinity   |              |
|            | 3. The filament used in incandescent lamp is made of<br>[a] copper                      [b] alluminium                      [c] nichrome                      [d] tongston   |              |
|            | 4. The value of crest factor is<br>[a] 11.1                      [b] 1.11                      [c] 1.414                      [d] 14.14  |              |
|            | 5. For a parallel resonance condition of a AC circuit current is<br>[a] minimum                      [b] maximum                      [c] zero                      [d] infinity   |              |
|            | 6. For unity power factor load of 3-phase ckt.,if we measure the power by 2-wattmeter method then readings of wattmeters are<br>[a] one wattmeter shows zero reading                      [b] equal & +ve sign<br>[c] equal & opposite sign                      [d] both shows zero reading   |              |
|            | 7. The power factor of R-C series Ac ckt. is<br>[a] unity                      [b] lagging                      [c] leading                      [d] zero  |              |

- Q.2** (a) State and explain ohm's law & its limitations. **03**  
 (b) Define & explain temperature co-efficient of resistance. **04**  
 (c) Derive the equations to translate a passive electric circuits from delta network to star network configuration with diagram. **07**
- Q.3** (a) Find out the equation for energy stored in capacitor. **03**  
 (b) Analyze the series and parallel connection of capacitor. **04**  
 (c) State and explain faraday's laws of electromagnetic induction. Prove the equations of self and mutual inductances for different methods. **07**
- Q.4** (a) State the points of differences in magnetic and electric circuits. **03**  
 (b) Analyze magnetic and electric circuits by similarities. **04**  
 (c) Analyze the phenomena of R-L-C series AC circuit with the help of equations & graph. **07**
- Q.5** (a) Define the following for AC circuits : **03**  
 [1] Form factor  
 [2] Amplitude factor  
 [3] Power factor  
 (b) An inductive circuit draws 10 A & 1 KW from 200 V, 50 Hz ac supply. Find **04**  
 [1] Z &  $X_L$   
 [2] power factor  
 [3] apparent power  
 [4] reactive power  
 (c) Prove the condition of resonance for R-L-C parallel AC circuit. Also analyze the phenomena with the help of graph. **07**
- Q.6** (a) Explain in brief the following for 3-phase AC circuit : **03**  
 [1] Line voltage  
 [2] Phase voltage  
 [3] Phase sequence  
 (b) For a balanced delta connected load supplied at 3-phase , 240 V ac supply , the two wattmeter readings are : (3210) & (-1710) W. Find out total power factor & current. **04**  
 (c) Prove the equation for measurement of Electrical power in 3-phase circuit by two wattmeter method for balanced load with phasor diagram. **07**
- Q.7** (a) Explain in brief the following. **03**  
 [1] A-h & W-h capacity of a battery  
 [2] ELCB  
 [3] Illumination  
 (b) Discuss the Lead acid battery with charging & discharging equations.. **04**  
 (c) What is Grounding & earthing ? Analyze concept of protection with a device-MCB used at our residence. **07**

\*\*\*\*\*