Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-IV (New) EXAMINATION - WINTER 2015

Subject Code:2140910			Date:22/12/2015	
Tiı	me: 2 tructio 1. 2.	t Name: Digital Electronics 2:30pm to 5:00pm Total Marks: ons: Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	70	
Q.1	(a) (b)	Give classification of binary codes with some example and short explanation. Define universal gate. Prove that NAND and NOR gates are universal gates.	07 07	
Q.2	(a)(b)(b)	Convert: (i) $(314.24)_8$ to () ₁₀ (ii) $(250.58)_{10}$ to () ₈ Explain in brief about error detection and correction codes. OR Simplify Y=A'BCD' + BCD' + BC'D' + BC'D and implement using NAND	07 07 07	
Q.3	(a) (b)	gates only. Explain CMOS NOR gate. Write short note on K-map.	07	
Q.3	(a) (b)	OR Explain two input TTL NAND gate. Express A'B + A'C as sum of minterms and also plot K-map.	07 07	
Q.4	(a) (b)	Write short note on half adder and full adder. What is positive and negative edge triggering? Explain SR flip flop with negative edge triggering. OR	07 07	
Q.4	(a) (b)	Explain multiplexer. Differentiate between excitation table and truth table. Write excitation table for J-K flip flop.	07 07	
Q.5	(a) (b)	Write a note on EEPROM. Explain working of ring counter.	07 07	
Q.5	(a) (b)	OR Explain binary weighted resistor digital to analog converter. Classify memory. Differentiate between RAM and ROM.	07 07	
