Seat No.:	Enrolment No.

Subject Code:2141003

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-IV (New) EXAMINATION - WINTER 2015

Date:28/12/2015

Subject Name: Electronics Measurement and Instrumentation Time: 2:30pm to 5:00pm Instructions: Total Marks:		70	
	1. 2. 3.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	Explain the following terms 1. Sensitivity 2. Reproducibility 3. Drift 4. Precision 5. Linearity 6. Dead time 7. Repeatability	07
	(b)	Explain Anderson bridge with vector diagram and also derives balance equation.	07
Q.2	(a)	Describe the working of a digital frequency meter with schematic block diagram.	07
	(b)	Draw the circuit of Kelvin's double bridge used for measurement of low resistance. Derive the condition for balance. OR	07
	(b)	Explain salient features of Maxwell's Inductance capacitance bridge. Draw phasor diagram and derive balance equation.	07
Q.3	(a) (b)	Explain True RMS Reading Voltmeter. Draw the block diagram of an oscilloscope and explain briefly its major system. OR	07 07
Q.3	(a)	Describe digital storage oscilloscope with schematic block diagram and state its Applications.	07
	(b)	Explain Vector Impedance Meter.	07
Q.4	(a) (b)	Explain harmonic distortion analyzer. Describe the working of a frequency synthesizer with schematic block diagram. OR	07 07
Q.4	(a) (b)	Explain frequency selective wave analyzer with block diagram. Describe the construction and working of L.V.D.T. with neat sketches. Draw its Output characteristics. State advantages and disadvantages of it.	07 07
Q.5	(a)	Explain the Principle of Hall effect and measure the displacement and current using Hall sensor.	07
	(b)	Explain the working of a Multi channel DAS with block diagram. OR	07
Q.5	(a) (b)	Explain the measurement of phase difference using X-OR and SR flip flop. Where are Sample and Hold circuits used? Sketch the circuit arrangement along with output waveforms and discuss briefly the operation of the circuit.	07 07
