GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-IV (New) EXAMINATION – WINTER 2015

Date:22/12/2015

Subject Code:2142405 Subject Name: AE&A Time: 2:30pm to 5:00pm

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Discuss diode as rectifier in bridge configuration along with C filter. Draw 07 necessary waveforms and figures.
 - (b) Brief switched capacitor circuit and explain MF5 switched capacitor filter. 07
- Q.2 (a) What is a filter? Explain first order bandpass filter with necessary equations 07 and waveforms.
 - (b) Explain triangular wave generator using Op-Amp. Give application of the 07 same.

OR

- (b) What are logic gates? Discuss their working principle. Explain TTL logic 07 family.
- Q.3 (a) Explain bistable multivibrator using 555. Give necessary equations and draw 07 neat figures and waveforms.
 - (b) Explain the block diagram and working of V/F converter.

OR

- Q.3 (a) Explain clipper and clamper circuit with necessary figure & waveforms. Give 07 applications of the same.
 - (b) Explain summing amplifier and scaling amplifier.
- Q.4 (a) What is Op-Amp? Draw its symbol and block diagram. Discuss the 07 characteristics of an ideal Op-Amp.
 - (b) Explain the design of a series regulated power supply. 07 OR
- Q.4 (a) Draw Op-Amp in differential configuration and explain its working. What 07 happens if the input of the Op-Amp is increased above its supply?
- Q.4 (b) Draw the block diagram of a linear regulated power supply and explain its 07 working.
- Q.5 (a) Explain Class B amplifier along with necessary figures, waveforms and 07 applications.
 - (b) Explain Op-Amp as summing amplifier. Give its applications. 07 OR
- Q.5 (a) Explain Class C amplifier with necessary figures, waveforms and applications. 07
 - (b) Explain 78xx and 79xx voltage regulators. Draw necessary figures and draw 07 circuit diagram to get 12 volt constant output using 7812 IC.

1

07

07

Total Marks: 70