GUJARAT TECHNOLOGICAL UNIVERSITY BE – SEMESTER – V (NEW) EXAMINATION – WINTER 2015

Subject Code: 2151707Date:17/12/2Subject Name: Microcontroller & InterfacingTime:10:30am to 1:00pmTime: 10:30am to 1:00pmTotal MarkInstructions:Total Mark			2015	
			70	
	1. 2. 3.	Make suitable assumptions wherever necessary.		
Q.1	(a) (b)	Compare the following: (i) Microprocessor and Microcontroller (ii) Absolute address decoding and Partial address decoding (i) Define: T-state, Machine cycle and Instruction cycle.	04 03 03	
		(ii) Explain with neat sketch how lower order address is demultiplexed in 8085.	04	
Q.2	(a) (b)	Interface the following memories with 8085: (i) 2K EPROM (ii) 2K RAM. The EPROM address should start from 0000H and the RAM address should begin at 4000H. Draw the complete interface diagram. Describe 8051 architecture with Block diagram.	07 07	
		OR		
	(b)	(i) Draw 8085 Bus structure.(ii) Explain in brief how four latches are configured as 4-bit registers.	03 04	
Q.3	(a)	Describe in detail the various addressing modes and assembler directives	07	
	(b)	supported by 8051 microcontroller with suitable examples. Write an assembly language program to convert a given binary number into its equivalent BCD code. Eg. $FF_H = 255_d$.	07	
Q.3	(a)	OR 8-SPST switches are connected to Port-3 of 8051. Assume that one of the switches is pressed. Write a program to display the no. of switch pressed on	07	
	(b)	seven segment display which is connected to Port 1. Draw the structure of SCON register and explain the importance of each bit. Write a C-program to transfer letter "M" serially at 4800 baud continuously.	07	
Q.4	(a)	Assuming that $XTAL = 22$ MHz, write an assembly language program to	07	
	(b)	generate a square wave of frequency 1 KHz on pin P1.3. Mention the various interrupts available in 8051. Explain in detail the IE(Interrupt Enable) register and IP(Interrupt Priority) Register. OR	07	
Q.4	(a) (b)	Draw and explain 8051 connections with MAX-232 and DB-9 connector. Describe in brief the different modes in 8255. Assume 8255 is connected with 8051 so that the addresses for Port A, Port B, Port C and Control Word Register are 4000H, 4001H, 4002H and 4003H respectively. Four switches are connected to lower 4-bit lines PB0-PB3. Write a program to transfer the status of these switches to LED's connected to upper 4-bits of Port A.	07 07	
Q.5	(a)	Interface 16x2 LCD with 8051. Write a C-program to display "WINTER	07	
	(b)	EXAM 2015", continuously. Explain with a neat sketch how a stepper motor is connected with 8051. Also write a C code to rotate it continuously.	07	

- Q.5 (a) Show 8051 connections with 4x4 Matrix Keyboard. Explain with the help of 07 flow chart the logic to identify the key pressed.
 - (b) Show 8051 connections with DAC 0808. Write a C-program to generate a 07 sine wave using the same.
