

GUJARAT TECHNOLOGICAL UNIVERSITY
BE - SEMESTER-1st / 2nd (SPFU) EXAMINATION- WINTER 2015

Subject Code: ENG005**Date: 22/12/2015****Subject Name: Linear Electrical Networks****Time: 10:30am to 01:00pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks

- Q.1** (a) Explain Kirchoff's current and voltage law. **07**
(b) Explain transformation of delta connected network into star connected network. **07**
- Q.2** (a) Explain Superposition theorem. **07**
(b) Explain Thevenin's theorem. **07**
- Q.3** (a) Explain initial conditions in circuit which contain resistor and inductor. **07**
(b) What is Laplace transform? Explain importance and applications of Laplace transform. **07**
- Q.4** (a) Explain hybrid parameters. **07**
(b) Explain series and parallel connection. Also compare them. **07**
- Q.5** (a) Explain series resonance condition in series RLC circuit. **07**
(b) Explain pole-zero construction of RLC series circuit. **07**
- Q.6** (a) Explain resonance condition in AC parallel circuit. **07**
(b) Explain loop, node, path, network and circuit. **07**
- Q.7** (a) Explain maximum power transfer theorem. Also discuss its advantages and disadvantages. **07**
(b) Explain the frequency domain behavior of one port passive network. **07**
