
Seat No.:	Enrolment No.

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

BE - SEMESTER- $1^{st}$  /  $2^{nd}$  (SPFU) EXAMINATION- WINTER 2015

Subject Code: TEE011 Subject Name: BASIC ELECTRONICS			
Tiı	me: ( tructio	02:30pm to 05:00pm Total Marks: 70 ons:	
	2.		
Q.1	(a)	Define active circuit element and passive circuit element. Explain Kirchhoff's Law with example.	07
	<b>(b)</b>	For given circuit diagram, find the current i <sub>1</sub> and i <sub>2</sub> as indicated. (See Fig. 1)	07
Q.2	(a) (b)	Explain in brief superposition theorem. Find the power loss in the $R_L$ =1 $\Omega$ Resistor by Thevenin's Theorem. (See Fig. 2)	07 07
Q.3	(a) (b)	Explain Wye –Delta transformation with suitable example. For the given circuit diagram, When $V_0=0$ , I=2A; Determine the value of current I when $V_0$ =10 using superposition theorem.(See Fig. 3)	07 07
Q.4	(a)	Draw the typical block diagram of Op-Amp and explain the functionality of each block.	07
	(b)	Draw the schematic symbol for the Op-Amp. Also Define the followings:  1) Input bias current 2) Common Mode Rejection Ratio 3) Slew Rate 4) Large signal voltage gain	07
Q.5	(a)	Draw the equivalent circuit of an Op-Amp and list the electric characteristics of the Ideal Op-Amp.	07
	<b>(b)</b>	Write a brief note on Summing and Averaging amplifier with circuit diagram inverting configuration.	07
Q.6	(a)	Draw the basic block diagram of computer system. Explain each block with its function.	07
	<b>(b)</b>	List the different digital system components. Explain any two with application point of view.	07
Q.7	(a)	What is OSI Model and explain the functioning of different layers of OSI Model.	07
	<b>(b)</b>	What are the different types of computer networks & explain in brief.	07

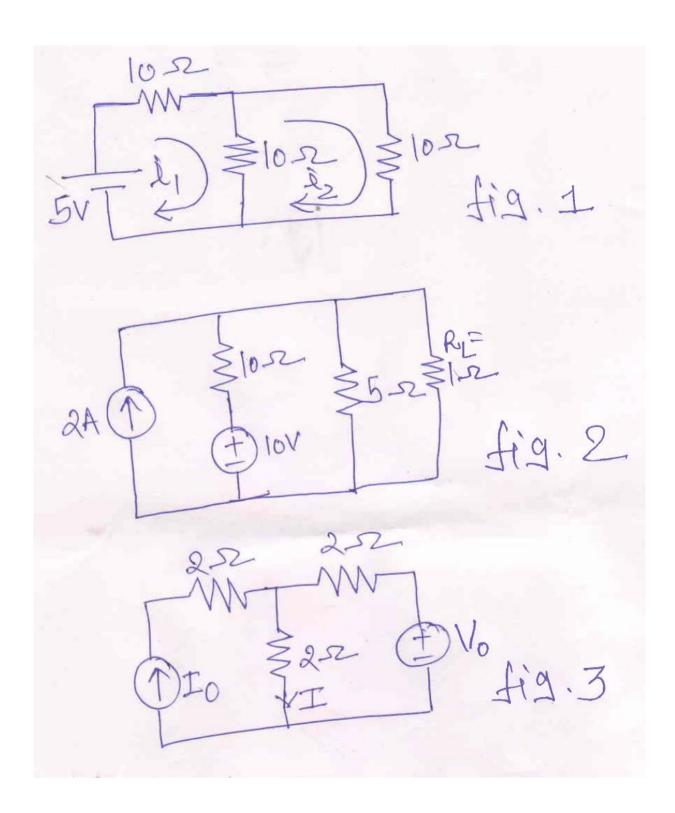

\*\*\*\*\*