

GUJARAT TECHNOLOGICAL UNIVERSITY
ME – SEMESTER II (OLD) – • EXAMINATION – SUMMER 2016


Subject Code: 1720709**Date: 20/05/2016****Subject Name: Advanced Power Converters****Time: 10:30 am to 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain the operation of series loaded resonant (SLR) half-bridge DC-DC converter operating in discontinuous mode. **07**
- (b) With the help of neat circuit and phasor diagram, derive the necessary equations for a Y/Z-1 configuration that helps to determine the number of turns to achieve the desired phase shift. **07**
- Q.2** (a) With relevant analysis show how harmonic cancellation occurs in a 12 pulse converter. Also, comment on the dominant harmonics in the line current and the output voltage. **07**
- (b) With neat waveforms discuss the operation of ZVS (Zero Voltage Switching) resonant switch converter. **07**

OR

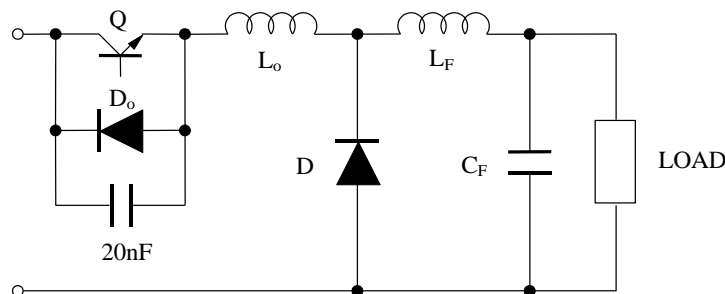- (b) The Zero Voltage Switching (ZVS) forward converter shown below works with a range of load currents from 5A to 15A. The supply voltage is 40V and the load voltage is 20V. You may assume that the output filter inductor current is smooth. **07**
- (i) Determine the value of L_o if it is chosen so that ZVS is just possible at the minimum load current.
- (ii) Calculate the converter operating frequency when operating at 5A output.
- (iii) Calculate the peak voltage across the transistor when operating at maximum load current.



- Q.3** (a) What factors lead to deviation of neutral-point voltage? How can this deviation be minimized in a three level diode clamped inverter? **07**
- (b) State the two basic rules to be observed for operating the switches of a Matrix converter and hence, group the possible switching state combinations of a 3-phase Matrix converter. Also, discuss the significance of LC filter in context to the converter. **07**

OR

- Q.3** (a) Write a brief note on over-voltage protection schemes of Matrix converter. **07**
- (b) Compare the two-step and four-step current commutation strategy for Matrix converter. **07**
- Q.4** (a) Draw the space vector diagram for diode-clamped 3-level inverter. Hence, derive the dwell time equations for the space vectors for any one region. **07**

- (b) Write a brief note on Flyback Capacitor multi-level inverter. **07**
)
- OR**
- Q.4** (a) Draw the configuration of SVC and STATCOM and compare them on various aspects. **07**
(b) With neat diagram, explain the control scheme for a STATCOM to provide reactive power compensation. **07**
)
- Q.5** (a) Write a brief note on the control of rectifier and inverter units of HVDC converter. **07**
(b) Draw I-V and P-V characteristics of a PV array and explain the effect of temperature and insolation on it. Also, define fill factor and discuss its significance for PV cell. **07**
)
- OR**
- Q.5** (a) With neat waveforms explain phase-shifted multi-carrier modulation control for five-level CHB multi-level inverter. **07**
(b) Discuss in brief MPPT control required for a Wind Energy Conversion System. **07**
)
