Seat No.: _____

Enrolment No._____

GUJARAT TECHNOLOGICAL UNIVERSITY ME – SEMESTER II (OLD) – • EXAMINATION – SUMMER 2016

]	ME – SEMESTER II (OLD) – • EXAMINATION – SUMMER 2016		
Subject Code: 1724101 Date:17/05/				
		ame: RF and Microwave Circuits		
Time:10:30 am to 01:00 pm Total Marks:			0	
Instru				
		Attempt all questions.		
		Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
	J. I	ngures to the right indicate iun marks.		
Q.1	(a) (b)	Explain smith chart with required equations. Define: Reflection coefficient, return loss, SWR, transmission coefficient. Discuss their significance when transmission line is short circuit, open circuit and matched.	07 07	
Q.2	(a)	Discuss single stub matching with suitable example	07	
	(b)	Derive the necessary equations for TE mode in a rectangular waveguide	07	
		OR		
	(b)	Explain microstrip line with equations of effective dielectric constant and characteristic impedance.	07	
Q.3	(a)	Explain Scattering matrix. Derive relation between scattering matrix with impedance matrix.	07	
	(b)	Explain signal flow graphs with four decomposition rules OR	07	
Q.3	(a)	Derive the equation of Q-factor for short circuited $\lambda/2$ lossy transmission line.	07	
	(b)	Explain directional couplers with S matrix	07	
Q.4	(a)	Explain power divider in details	07	
_	(b)	Explain quadrature hybrid junction.	07	
		OR		
Q.4	(a)	Explain Ferrite isolator	07	
	(b)	Explain analysis of infinite periodic structure	07	
Q.5	(a)	Explain filter design by image parameter method	07	
	(b)	Explain Richard's transformation for filter implementation	07	
Q.5	(a)	OR Explain microwave mixer circuits with suitable example	07	
Q.3	(a) (b)	What do u mean by microwave oscillator? Explain any one microwave oscillator.	07 07	
