Sea	at No.:	Enrolment No	
		GUJARAT TECHNOLOGICAL UNIVERSITY	
C		ME – SEMESTER II (OLD) – • EXAMINATION – SUMMER 2016	17
Subject Name: Power Electronics-II			16
			70
	tructio	ons:	
	2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	Explain need of 3-Ø to 3-Ø Matrix Converter with necessary circuit and Switching Matrix Diagram.	07
	(b)	Explain problem associated with respect to Power Factor in Single Phase Line Commutated Rectifier. Suggest topology to overcome associated problem. Draw necessary Circuit and Waveform in support.	07
Q.2	(a)	The Class E Resonant Inverter has $Vs=12$ Volts and $R=10$. The Switching Frequency $fs=25$ KHz. Determine: (a) the Optimum values of L, C, Ce and Le, (b) Damping Factor and (c) Resonant Frequency. Assume $Q=7$.	07
	(b)	Explain operation of Six Pulse Bridge Converter, having Resistive Load, with necessary Power Circuit and Waveforms. OR	07
	(b)		07
Q.3	(a)	With respect to Magnetic Component Design explain importance of Hysteresis Loss. Support answer with suitable diagram.	07
	(b)	Explain design procedure for Inductor. Draw necessary Flow chart in context of answer.	07
Q.3	(a)	OR With respect to Magnetic Component Design explain importance of Skin Effect. Support answer with suitable diagram.	07
	(b)	Explain design procedure for Transformer. Draw necessary Flow chart in context of answer.	07
Q.4	(a)	Explain Series loaded dc-dc Resonant Converter in Continuous Conduction Mode. Draw necessary Circuit and Waveforms in support.	07
	(b)	Explain Zero-Voltage Switching Resonant Converter. Draw various Switching Configuration with necessary Waveforms in support. OR	07
Q.4	(a)	Explain Parallel loaded dc-dc Resonant Converter in Continuous Conduction Mode. Draw necessary Circuit and Waveforms in support.	07

(b) Explain Resonant DC Link Inverter with necessary Circuit and Waveforms.

Q.5 (a) Explain operation of Neutral Point Clamped Multilevel Inverter. Draw neat labeled diagram in support

07

07

(b) List various Control Strategies for Power Converters. Explain sliding Mode 07 Control in context of the same.

OR

- Q.5 (a) Explain operation of Cascade type Multilevel Inverter. Draw neat labeled 07 diagram in support
 - (b) Explain operation of Single Phase Boost Rectifier as Power Factor Conversion
 Topology. Draw necessary circuit in support.
