Se	at No.:	Enrolment No	
Ç.	.hiaat	GUJARAT TECHNOLOGICAL UNIVERSITY ME – SEMESTER II (NEW) – • EXAMINATION – SUMMER 2016 Code: 2720721 Date: 21/05/2016	<i>(</i>
	•	Code: 2720721 Date: 31/05/2010 Name: Application of Power Electronics to Power System	O
	-	2:30 am to 01:00 pm Total Marks: 7	0
Ins	1. 2. 3.		
Q.1	(a)	Derive the expression of power for a lossless transmission line. Use usual notations. Also, explain why absorption and generation of reactive power are not equal in the line unlike active power.	07
	(b)	Explain the effect of series compensation on power transfer capacity of transmission line. What are the key factors which need to be considered seriously for the application of series compensation?	07
Q.2	(a)	Explain the role of phase-shifting transformer in context of conventional control	07
	(b)	mechanism. Define and explain following in brief. a) SVC b) FACTS controller c) UPFC d) IPFC OR	07
	(b)	Explain Multilevel VSC-Based STATCOM and state its salient features.	07
Q.3	(a)	For a given 765 kV, 50 Hz, 700 km long, symmetrical lossless transmission line with l =0.85 mH/km, $c = 13.1$ nF/km mid-point compensated line, find uncompensated real power (P_s), compensated real power (P_{comp}) with unlimited capacity compensator at midpoint for mid point voltage of 1.02 pu and injected reactive power (Q_v). The value of load angle δ is 30°. Also, comment on results.	07
	(b)	Draw and explain voltage-current characteristic of a TCR without voltage controller.	07
Q.3	(a)	OR For a given 1200 kV, 50 Hz, 1000 km long, symmetrical transmission line with	07
Ų.J		l =0.87 mH/km, c = 14.1 nF/km mid- point compensated line the realistic midpoint VAR compensator is incorporated and rated to operate from -750 to 0 MVAR. Find the working operating range for mid-point voltage and operating load angle δ . V_{mc} is to be held at 1.015 pu. Also, comment on result.	
	(b)	Draw and explain operating characteristic of a TCR with voltage controller.	07
Q.4	(a)	Draw and explain IEEE first benchmark system and its components. List methods used for analysis of SSR and explain any one in detail.	07
	(b)	Compare STATCOM and synchronous condenser. OR	07
Q.4	(a)	Explain the working principle of UPFC and its various modes of operation with	07
	(b)	suitable applications. Explain the principle of operation of SSSC and various operating modes for power exchange.	07

Explain the basic principle of TCSC. Also explain different modes of TCSC

voltage across inductor for firing angle $\alpha = 90^{\circ}$, $\alpha = 150^{\circ}$ and $\alpha = 180^{\circ}$.

operation.

Q.5

(a)

(b)

Draw the waveforms of current through TCR, voltage across thyristor and

07

07

- Q.5 (a) Explain the basic concepts of NGH-SSR damping scheme.
 (b) Explain how collapsing of voltage is taken care in TCSC installed line. What is
 07
 - (b) Explain how collapsing of voltage is taken care in TCSC installed line. What is the significance of performance factor?
