

GUJARAT TECHNOLOGICAL UNIVERSITY
ME – SEMESTER II (NEW) – • EXAMINATION – SUMMER 2016

Subject Code: 2722914**Date: 02/06/2016****Subject Name: Industrial Electronics & Control****Time: 10:30 am to 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Notations/ symbols used have usual meanings.

- Q.1 (a)** Draw block diagram of on-line UPS system and explain its operation. Why battery backup is required in UPS system? **08**
- (b)** Differentiate: (i) POWER TRANSISTOR ó POWER MOSFET. **06**
(ii) Induction Heating ó Dielectric Heating
- Q.2 (a)** Discuss SMPS design for push-pull type topology. **07**
- (b)** A copper conductor has a circular cross-section 5cms in diameter. Calculate the resistance per meter length of the cylinder at 10kHz. Assume conductivity of copper is 5.7×10^7 S/m. **07**
- OR**
- (b)** Derive an expression for the power density for dielectric heaters. **07**
- Q.3 (a)** Draw detailed V-I characteristics of the SCR and explain the utility of Latching and Holding current. **07**
- (b)** Describe operation of a sequence timer used for an automatic welding process. **07**
- OR**
- Q.3 (a)** Discuss electronic welding controls used in resistance welding. **07**
- (b)** Explain switching characteristic of IGBT. State advantages of IGBT. **07**
- Q.4 (a)** Where variable - speed synchronous motors are used? Discuss performance of voltage source inverter drive with open loop control. **07**
- (b)** Discuss the closed loop control ó PLL scheme to control DC motor **07**
- OR**
- Q.4 (a)** Explain stator voltage controller and draw the motor and load torque ó speed characteristics for voltage control. **07**
- (b)** Discuss the control of DC motor using chopper. **07**
- Q.5 (a)** Write short note on: Use of SCRs in HVDC transmission **07**
- (b)** Write short note on: Static circuit breaker. **07**
- OR**
- Q.5 (a)** Explain in brief- Battery operated vehicle. **07**
- (b)** Write short note on: Servo Controlled Voltage stabilizer. **07**
