Enrolment No.____

GUJARAT TECHNOLOGICAL UNIVERSITY

ME – SEMESTER II (NEW) – • EXAMINATION – SUMMER 2016

Subject Code: 2724407 Date: 31/05/2016 Subject Name: VLSI in Wireless Communication systems Time:10:30 am to 01:00 pm

Total Marks: 70

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- (a) Explain the operations of QPSK modulator and demodulator with block diagrams. Q.1 07
 - 07 (b) For noisy two port networks of K- stages, each with noise derive equation for Noise figure.
- Q.2 (a) Draw heterodyne architecture of RF receiver and also explain the functions of 07 Band selection filter, Image rejection filter and channel filter.
 - (b) Explain the operations of BPSK modulator and demodulator with block diagrams. 07

OR

	(b)	Write short note on types of circuit noise.	07
Q.3	(a)	What is frequency synthesizer? Explain PLL based frequency synthesizer.	07
	(b)	Explain the multipath fading in details	07
		OR	
Q.3	(a)	Describe CMOS based XOR- Phase detector in detail	07
	(b)	Discuss for receiver design, the effects of non idealities into the corresponding design parameters	07
Q.4	(a)	Explain with neat diagram CMOS based ring Oscillator	07
	(b)	Describe the operation of Gillbert mixer in detail along with neat diagram.	07
		OR	

Q.4	(a)	Make comparisons between Wide band and Narrow band LNA.	07
	(b)	Describe the operation of charge pump in detail.	07

Q.5	(a)	Mention the design steps for CMOS sigma delta ADC	07
	(b)	Explain the operations of FSK modulator and demodulator with block diagrams.	07
		OR	
Q.5	(a)	Define the term "channel " for communication and describe AWGN in channel	07
	(b)	Describe the function of CMOS based Sample and Hold circuit in ADC	07
