GUJARAT TECHNOLOGICAL UNIVERSITY

ME –	- SEMESTER	III (NEW) – •	EXAMINATION -	- SUMMER 2016
				-

	•	Code: 2732903 Date:03/05/20 Name: Power Electronics for Power System	16	
Time:10:30 am to 01:00 pm Total Marks				
Inst	1. 2. 3.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a) (b)	Define FACT controllers. Explain the basic types of FACT controller. Give the expression for active and reactive powers in terms of d-q components.		
Q.2	(a) (b)	Explain advantage and application of FACT controller. Discuss Instantaneous reactive power theory. OR	07 07	
	(b)	Discuss Reference frame theory.	07	
Q.3	(a) (b)	Explain the principle and operation of STATCOM with its characteristics. Discuss the operation of Thyristor controlled reactor (TCR) along with its characteristic.	07 07	
0.3	(a)	OR Explain operation of Fixed Capacitor Thyristor Controlled Reactor (FC-TCR) with	07	
Q.3	(a) (b)	neat diagram. Write a short note on Static VAR Compensator (SVC).	07 07	
Q.4	(a)	What is objective of series compensator? Give the comparison between Series and	07	
	(b)	Shunt compensator. Write a short note GTO Controlled Series Capacitor (GCSC). OR	07	
Q.4	(a) (b)	Write a short note on Thyristor Controlled Series Capacitor (TCSC). Explain Static Synchronous Series Compensator (SSSC) with neat diagram		
Q.5	(a)	Explain the operation of Unified Power Flow Controller (UPFC) with vector	07	
	(b)	diagram Discuss Constant extinction angle and Constant ignition angle control in HVDC system.	07	
Q.5	(a)	OR Discuss Individual phase control and Equidistant firing angle control in HVDC	07	
Q.3	(a)	system.	07	
	(b)	With diagram explain Multi pulse bridge converter in HVDC system.	07	
