Seat No.:	Enrolment No
-----------	--------------

GUJARAT TECHNOLOGICAL UNIVERSITY

ME - SEMESTER III (NEW) - • EXAMINATION - SUMMER 2016

Subject Code: 2734501 Date:03/05/2016 **Subject Name: Application of Power Electronics to Power System** Time: 10:30 am to 01:00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. Draw and explain dynamic V-I characteristics of SVC and voltage-reactive 0.1 (a) **07** power characteristic of SVC. **(b)** With the help of circuit and phasor diagram explain system compensation and **07** load compensation. **Q.2** (a) Explain load sharing between parallel connected SVCs with diagram. 07 Write a short note on synchronous condenser. **(b)** 07 Briefly describe the working of a Thyristor Controlled Transformer (TCT). **07 (b)** 0.3 Giving circuit diagram, explain the working of series active filters. Also discuss **07** (a) the algorithm used to generate compensated voltage signals. Explain briefly operation of Thyristor Switched Capacitor (TSC). **(b)** 07 **Q.3** Explain briefly operation of Thyristor Controlled Rectifier (TCR). 07 (a) Explain working of shunt active filter for constant power compensation. Draw **(b)** 07 the block diagram for constant instantaneous power control strategy and explain its working. Discuss the reduction in the SVC reactive power rating by current slope. 07 **Q.4** (a) Discuss the role of SVC as a voltage regulator with diagram. **(b)** 07 **Q.4** Discuss the role of SVC as a voltage controller with diagram. 07 (a) Draw and explain reactance (X_{TCSC}) Vs thyristor firing delay angle (α) **07 (b)** characteristics of TCSC. Q.5 (a) Explain principle of operation of UPFC with relevant phasor diagram and 07 describe its implementation using back to back VSCs with schematic diagram. Explain with the help of suitable diagram working principle of STATCOM and **(b)** 07 it V-I characteristic. Explain the principle of operation of Static Synchronous Series Capacitor Q.5 **07** (SSSC) scheme. Explain the application of STATCOM for improving transient stability of a 07 **(b)** power system. *****