Seat No.:		Enrolment No.		
		GUJARAT TECHNOLOGICAL UNIVERSITY ME – SEMESTER I (OLD) – • EXAMINATION – SUMMER 2016		
Subject Code: 710702N Date:		Code: 710702N Date:17/05/20	17/05/2016	
	•	Name: Advanced Power Electronics		
Time:02:30 pm to 05:00 pm Total M		: 70		
Ins	tructio			
	1. 2. 3.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a) (b)	Discuss static and dynamic characteristics of power MOSFET and IGBT. Compare buck and boost regulators. Explain working of boost regulator with necessary circuit and waveforms.	07 07	
Q.2	(a)(b)	Explain the functions of dc-dc converter. Explain the working of Buck regulators with the help of circuit diagram and various waveforms. What is the need of isolation in driver circuit? Discuss the basic two ways of isolating gate signal.	07 07	
		OR		
	(b)	Distinguish between SCR, GTO and Power BJT.	07	
Q.3	(a)	State the advantages of Switched –Mode DC power supplies. With neat diagrams and waveforms, analyze operation of Fly-back converters.	07	
	(b)	Write short note on SMPS design criterion. OR	07	
Q.3	(a) (b)	Compare voltage source inverter and current source inverter. Discuss (i) harmonic reduction by PWM to eliminate a pair of harmonics and (ii) harmonic reduction by transformer connection methods.	07 07	
Q.4	(a)	Derive the expression for the r.m.s. output voltage of a 3-phase, 3-wire star connected AC controller with resistive load. Also draw the necessary circuit	07	

Explain the basic principle of operation of a cycloconverter with a neat circuit

OR

What is the difference in design of power transformer and high frequency

State the main requirements and advantages of a good current transformer. Also

Compare 120⁰ and 180⁰ of firing schemes in a 3-phase inverter. Discuss any one

diagram. Derive the equation of the fundamental r.m.s. value of per phase

output voltage of low frequency for an m-pulse cycloconverter.

Explain operation 3-phase full wave controllers with resistive loads.

Discuss circulating current operation of 3-phase cyclo-converter.

Discuss C'uk converter with suitable diagram and waveforms.

in details with the help of necessary diagram and waveforms.

and waveforms for firing angle of 60° .

state different types of magnetic core materials.

(b)

(a)

(b)

(a)

(b)

(a) (b) transformer?

Q.4

Q.5

Q.5

07

07

07

07

07

07

07