Enrolment No.

Date:17/05/2016

Total Marks: 70

GUJARAT TECHNOLOGICAL UNIVERSITY ME – SEMESTER I (OLD) – • EXAMINATION – SUMMER 2016

Subject Code: 712902N

Subject Name: Power Processing Circuits

Time:02:30 pm to 05:00 pm

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- 4. Notations used have usual meaning.

0.1	(a)	Explain construction and working of power MOSFET device in detail.	07
V •1	(a)	Explain construction and working of power most E1 device in detail.	07

- (b) What is safe operating area? Discuss SOA for bipolar junction transistor. 07
- Q.2 (a) Compare Integral cycle control with phase angle control for AC-AC control in 07 all respect.
 - (b) Explain single phase to single phase Cyclo-converter with discontinuous 07 current operation.

OR

- (b) Explain three phase half wave controlled AC-DC converter circuit with 07 waveforms.
- Q.3 (a) Explain working operation of dual converter with circulating mode. Draw 07 appropriate waveforms.
 - (b) Discuss the working of DC-DC boost converter with appropriate waveforms. 07

OR

- Q.3 (a) Explain working of three phase inverter circuit with 120 conduction mode. 07 Draw line voltage and phase voltage waveform.
 - (b) Discuss working operation of buck-boost DC-DC converter circuit with 07 appropriate waveforms.
- Q.4 (a) Write a short note on ring connected Cyclo-converter circuit. 07
 - (b) Explain single pulse width modulation technique for single phase inverter 07 circuit. Draw necessary waveforms.

OR

- Q.4 (a) Explain working principle of single phase AC-AC controlled converter with 07 necessary waveforms.
 - (b) Write a brief note on effect of source inductance on AC-DC converter. 07
- Q.5 (a) Explain working of single phase semi-controlled converter with R-L load. 07 Draw necessary waveforms.
 - (b) Discuss full bridge DC-DC converter with appropriate waveforms. 07

OR

- Q.5 (a) Write a short note on harmonics reduction in output of the inverter circuit. 07
 - (b) Explain sinusoidal pulsed width modulation technique for inverter. 07
