GUJARAT TECHNOLOGICAL UNIVERSITY ME – SEMESTER I (OLD) – • EXAMINATION – SUMMER 2016

Subject Code: 714501N

Date:16/05/2016

Subject Name: Power Electronics - I

Total Marks: 70

Time:02:30 pm to 05:00 pm Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- **3.** Figures to the right indicate full marks.
- 4. .
- 5. Notations and symbols used have usual technical meaning.

Q.1 (a) Explain principle of operation of Power MOSFET with neat diagrams. (b) Explain the operation of 3-phase bridge inverter with Y-connected resistive 07 load in 120° conduction mode with neat circuit diagram and waveforms.

- Q.2 (a) Explain Class-C commutation of SCR with necessary waveforms. 07
 - (b) Explain the operation of buck converter with necessary waveforms. 07 OR
 - (b) Explain principle of operation of IGBT with neat diagrams. 07
- Q.3 (a) Explain bipolar switching scheme of a 1-phase sinusoidal PWM inverter 07 with neat circuit diagram and waveforms.
 - (b) Explain center-tapped 1-phase to 1-phase cycloconverter with neat circuit 07 diagram and waveforms.

OR

- Q.3 (a) Draw only the basic structure of a TRIAC. Enlist all the possible triggering 07 modes of TRIAC. Explain any one triggering mode.
 - (b) Explain the operation of a 6-pulse converter with neat circuit diagram and 07 waveforms.
- Q.4 (a) Explain the operation of push-pull converter with neat circuit diagram and 07 necessary waveforms.
 - (b) Explain dual converter with circulating current control mode. 07
 - OR
- Q.4 (a) Explain 2-transistor model of SCR and derive the expression of anode 07 current.
 - (b) Explain the need of Heat-sink. Explain its selection process. 07
- Q.5 (a) Draw only the structure and V-I characteristic of Power BJT. Explain its 07 various operating modes.
 - (b) Explain the principle of operation of integral cycle control type 1-phase 07 AC voltage controller with neat diagram and waveforms. Also derive the expression for the RMS output voltage in terms of duty cycle.

OR

- Q.5 (a) Explain the operation of forward converter with neat circuit diagram and 07 necessary waveforms.
 - (b) Explain any one harmonic elimination technique with respect to 1-phase 07 inverter.
