Enrolment No._____

GUJARAT TECHNOLOGICAL UNIVERSITY ME - SEMESTER- II(Old course) • EXAMINATION (Remedial) – WINTER- 2015

Subject Code: 1724501 Subject Name: SOLID STATE AC DRIVES Time:2:30 pm to 5:00 pm Instructions:

Date: 09/12/2015

Total Marks: 70

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Sketch a typical torqueóspeed curve for an induction machine, covering the range of slips from 2 to -1. Identify the motoring, generating and braking regions. Which quadrants of the torqueóspeed plane are accessible when an induction machine is operating from a constant voltage and constant frequency supply?
 - (b) Compare voltage control, rotor resistance and frequency control methods for 07 speed control of induction motor. Give the suitable applications of each speed control method.
- Q.2 (a) Draw the block diagram of static voltage controlled three phase induction 07 motor drive for closed loop operation. Explain the function of each block.
 - (b) With diagram describe operation of the static slip power recovery scheme for 07 an induction motor.

OR

- (b) Explain the variable frequency speed control method of VSI fed three phase 07 induction motor. Explain the necessity to maintain constant V/F ratio.
- Q.3 (a) What is the effect of motor inductance on VSI and CSI fed induction motor 07 drive. State the advantages of CSI fed induction motor drive over VSI fed drive.
 - (b) Explain field oriented control of induction motor. Write benefits of the 07 method with justifications.

OR

- Q.3 (a) Draw the block diagram of closed loop CSI fed three phase induction motor 07 drive. Explain the function of each block.
 - (b) Explain indirect vector control of induction motor with current model.
- Q.4 (a) How direct torque control method differs from field oriented control of 07 Induction Motor? Specify advantages and applications of DTC.
 - (b) A three-phase, 11.2 kW, 1750 rpm, 460 V, 60 Hz, four pole, Y-connected induction motor has the following parameters : Rs = 0.1 Ohm, Rrø= 0.38 Ohm, Xs=1.14 Ohm, Xrø=1.71 Ohm, and Xm =33.2 Ohm. If the breakdown torque requirement is 35 Nm, Calculate : a) the frequency of supply voltage, b) speed of motor at the maximum torque

OR

- Q.4 (a) Derive torque equations of Induction motor with stator and rotor flux for 07 DTC.
 - (b) Briefly explain brush and brushless excitation for wound field synchronous 07 machine drives.

1

07

- Q.5 (a) Explain self-controlled synchronous motor drive employing load commutated 07 thyristor inverter.
 - (b) List out different methods for speed estimation of Induction Motor. Draw the block diagram of sensorless vector control method for Induction Motor.

OR

- Q.5 (a) Explain power factor control of synchronous motor with changing excitation 07 for constant load torque.
 - (b) What is self-controlled and true synchronous mode of variable frequency 07 controlled synchronous motor?
