GUJARAT TECHNOLOGICAL UNIVERSITY ME - SEMESTER-I(New course)• EXAMINATION – WINTER- 2015

Subject Code: 2710702 Date: 02/01/2016 **Subject Name: Power Electronics** Time: 2:30 pm to 5:00 pm **Total Marks: 70** Instructions: 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. 07 **Q.1 (a)** Discuss Static Anode cathode characteristic and Gate characteristic of SCR What is the need of Electrical Isolation in Power Electronics? Give the basic 07 **(b)** ways to provide electrical Isolation. Also explain any one in brief. Explain Cuck Converter with necessary waveforms. Also derive the output **O.2** (a) 07 voltage. Discuss Sepic Converter with necessary waveforms. 07 **(b)** OR **(b)** Discuss Push-Pull converter for discontinuous conduction mode operation with 07 relevant waveforms. Explain the operation of 3- phase inverter for 150 degree conduction mode Q.3 07 (a) with necessary waveforms. **(b)** What is the effect of source inductance on three phase half wave controlled 07 converter? discuss briefly with necessary waveforms OR Q.3 Discuss the conversion and Inversion mode of 3-phase full controlled 07 **(a)** converter. **(b)** Short Note on Three phase dual Converter. 07 Why should we controlled or eliminate the harmonic components? Give the 07 **Q.4 (a)** various harmonic reduction or controlled techniques. Also explain any one. Discuss the 3-phase CSI with Commutation capacitance. 07 **(b)** OR Give the Control strategies of AC Voltage controller. Also explain any one **Q.4 (a)** 07 with necessary derivation and waveforms. Explain 3-phase 3-wire AC regulator for α =120° with relevant waveforms. 07 **(b)** Also find out RMS output voltage. Q.5 **(a)** Short Note on DC link Converter. 07 Describe 3-Ø to 1-Ø cyclo converter with relevant waveforms. 07 **(b)** OR Write short note on design criteria of SMPS Q.5 07 **(a) (b)** Why Blanking Times is provided in Bridge Circuit explain briefly. 07
