

GUJARAT TECHNOLOGICAL UNIVERSITY
ME - SEMESTER-I(New course)• EXAMINATION – WINTER- 2015

Subject Code: 2710709**Date: 04/01/2016****Subject Name: Electrical Drives****Time:2:30 pm to 5:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Describe the various components of load torques. **07**
 (b) i. Explain factors affecting the ratings of converters and motors with help of speed-torque characteristics. **07**
 ii. Explain speed transition from lower speed to higher speed in four quadrant drive. Comment on performance in context of ratings of drive.
- Q.2** (a) Explain DC dynamic braking of induction motor and derive expression of maximum braking torque. **07**
 (b) A 220V, 1400 rpm, 12A separately excited motor is controlled by a 1-phase fully controlled rectifier with an ac source voltage of 230A, 50Hz. Armature resistance and inductance are $R_a = 1.8\Omega$ and $L_a = 30\text{mH}$, respectively. **07**
 i. What should be the value of the firing angle to get the rated torque at 950 rpm?
 ii. What would be motor torque for $\alpha = 60^\circ$ and speed = 375rpm.
- OR**
- (b) A 220V, 1400 rpm, 12A separately excited motor is controlled by a 1-phase fully controlled rectifier with an ac source voltage of 230A, 50Hz. Armature resistance and inductance are $R_a = 1.8\Omega$ and $L_a = 30\text{mH}$, respectively. **07**
 i. Calculate the firing angle for the rated braking torque and -1400rpm?
 ii. What would be motor torque for $\alpha = 60^\circ$ and speed = 950rpm.
- Q.3** (a) Explain motoring Mode-I (conventional) and Mode-III (with controlled fly wheeling) operation of 1-phase fully controlled rectifier-fed DC separately excited motor. **07**
 (b) Explain the Sine-PWM modulation technique for 1-phase fully controlled rectifier. **07**
- OR**
- Q.3** (a) Explain Mode-V (conventional) and Mode-VII (with controlled fly wheeling) operation of 1-phase fully controlled rectifier-fed separately excited motor for regenerative braking action. **07**
 (b) Draw and explain closed loop armature control scheme with field weakening of separately excited DC motor. **07**
- Q.4** (a) Write a brief note on modified Kramer drive. **07**
 (b) Derive the expression of speed for time ratio control (TRC) using steady state analysis for chopper controlled DC separately excited motor. Explain its benefits and limitations. **07**
- OR**
- Q.4** (a) Explain the principle of operation of a Static Scherbius drive. Also, discuss the possible modes of operation with the scheme. **07**
 (b) Compare current source and voltage source inverter induction motor drives. **07**
- Q.5** (a) Explain the use of induction motors in fan and pump drives applications and **07**

derive expression for ratio of maximum to rated motor current.

- (b) Draw and explain Current-Source-Inverter variable frequency drive with slip speed control. **07**

OR

- Q.5** (a) Discuss the method for injection of voltage in the rotor circuit to control the speed of an induction motor in a super-synchronous region. **07**
- (b) What is Dual converter? Draw and explain how the circulating current is controlled in dual converter with simultaneous control. **07**
