GUJARAT TECHNOLOGICAL UNIVERSITY

ME - SEMESTER-I(New course) • EXAMINATION - WINTER- 2015

Subject Code: 2713108		Code: 2713108 Date: 01/01/20	Date: 01/01/2016	
Sul	bject	Name: Medical Instrumentation & systems		
Time: 2:30 pm to 5:00 pm Total Mai		70		
Inst	1. 2. 3.	Attempt all questions.		
Q.1	(a)	Enlist Static Limitations of Operational Amplifier and explain any two of them in detail.	07	
	(b)	Explain switched capacitor type filter in detail with its necessary circuit and equations.	07	
Q.2	(a)	Design and derive the necessary equation for the signal conditioning circuit to convert the current in to its equivalent voltage. How can we improve the sensitivity of I-V converters?	07	
	(b)	Enlist Electrical Safety issues in Biomedical Instrumentation system. Discuss any three in details.	07	
	(b)	OR State merits of using Low noise of amplifier over conventional amplifier in medical instrumentation. Explain briefly Low noise amplifier with its necessary equation.	07	
Q.3	(a)	What is need of Isolation of Amplifier in Biomedical Instrumentation? Explain it with any application.	07	
	(b)	What is the importance of using Instrumentation amplifier in biomedical application? Derive equation of gain for instrumentation amplifier. OR	07	
Q.3	(a)	Write an introductory notes on Modulation and Demodulation techniques for Biomedical Signals.	07	
	(b)	Differentiate between active filters and passive filter. Explain first order high pass active filter with its overall gain equation.	07	
Q.4	(a)	What are the sources of random noises in medical instrumentation system? Give their properties.	07	
	(b)	Write Short on voltage controlled oscillators with necessary schematic and equations. Explain its importance in medical instrumentation. OR	07	
Q.4	(a) (b)	Draw and explain the noise equivalent circuit for the BJT amplifier. Write Short on Current controlled oscillators with necessary schematic and equations. Explain its importance in medical instrumentation.	07 07	
Q.5	(a)	Explain working of weighted capacitor type DAC. Derive relation between analog output and digital input.	07	
	(b)	Give statistical related to noise in Resistors. OR	07	
Q.5	(a)	Explain working of successive approximation type ADC.	07	
-	(b)	Explain two-noise source model for a noisy amplifiers	07	
