Enrolment No._____

GUJARAT TECHNOLOGICAL UNIVERSITY ME - SEMESTER- II(New course) • EXAMINATION (Remedial) – WINTER- 2015

Subject Code: 2720709Date: 10/12/2015Subject Name: Advanced Power ConvertersTime:2:30 pm to 5:00 pmInstructions:Total Marks: 70

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) With relevant waveforms explain the operation of Half Bridge PLR dc-dc 07 converter when operating with $_{s} < _{o}/2$.
 - (b) State the advantages of multi-level inverter. Draw the space vector diagram 07 for three-level NPC inverter. Show the analysis for the orientation and magnitude of the space vectors representing *POPøand PNOø* combinations.
- Q.2 (a) The SLR dc-dc converter has the following parameters for its components: Cr 07 = 0.1μ F and Lr = 100μ H, output capacitor Co = 2000μ F. The input source Vd is 24V and the output voltage, Vo is 5V. The switching frequency is 20 kHz. Identify the mode of operation for this converter. Determine (a) peak value of the resonant inductor current and (b) peak value of the voltage across the resonant capacitor.
 - (b) For Y-Z1 phase-shift configuration, derive the equation of the input side line 07 current in terms of secondary side line current. Consider N1 = 1 pu, primary to secondary side line voltage ratio = 1 and phase shift between secondary and primary side line voltage = 15° .

OR

- (b) Discuss the significance of a phase shifting transformer for a multi-pulse 07 converter application. With detailed mathematical analysis for any one appropriate phase shifting transformer configuration explain how a phase shift of -15° can be obtained.
- Q.3 (a) What factors lead to deviation of neutral-point voltage? How can this 07 deviation be minimized in a three level diode clamped inverter?
 - (b) With neat waveforms discuss the operation of ZCS switched dc-dc Buck 07 converter.

OR

- Q.3 (a) With neat waveforms discuss the operation of ZVS-CV (Zero Voltage 07 Switching-Clamped Voltage) dc-dc converter.
 - (b) State the two basic rules to be observed for operating the switches of a 07 Matrix converter and hence, group the possible switching state combinations of a 3-phase Matrix converter. Also, discuss the significance of LC filter in context to the converter.
- Q.4 (a) Critically evaluate the various popular level-shifted carrier based PWM 07 techniques used for multi-level inverter.

(b) Explain the control and operation of FC-TCR for reactive power 07 compensation with neat circuit diagram and waveforms.

OR

- Q.4 (a) How can one get more than 5 levels from two H-bridge connected in 07 cascade? Show the maximum possible levels that one can get with this arrangement and also list the switch combinations and corresponding level of output voltage.
 - (b) Write a brief note on instantaneous reactive power compensation using 07 FACTS devices.
- Q.5 (a) Draw a one line diagram of an HVDC transmission system for interconnecting 07 two ac systems. Also explain the functions of each component involved in it.
 - (b) With the help of relevant characteristics, discuss in brief the need of MPPT 07 control of a Wind Energy Conversion System.

OR

- Q.5 (a) Write a brief note on any one control strategy for matrix converter. 07
 - (b) PV module with following rating is available

07

 $V_{oc} = 21V$ and $I_{sc} = 3.8A$.

Two such modules are connected in series and are feeding a resistive load of 10 through a dc-dc converter. Out of Buck and Boost converter which converter one should select to extract maximum power from PV array. Give detailed justification.
