GUJARAT TECHNOLOGICAL UNIVERSITY ME - SEMESTER- II(New course) • EXAMINATION (Remedial) – WINTER- 2015

	•		Date: 08/12/2015 Total Marks: 70	
Tin	•			
Inst	1. 2. 3.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. Notations used have usual meaning.		
Q.1	(a) (b)	Explain basic concept of soft switching. Describe ZCS type Buck converter with neat diagram and appropriate waveforms. Explain working operation of Single-Switch Forward Converter with neat diagram and appropriate wave.	07 07	
Q.2	(a) (b)	Explain Diode clamp type multilevel converter circuit. Write a short note on high frequency isolation transformer used in DC-DC converter. OR	07 07	
	(b)	Describe working operation of Fly back converter.	07	
Q.3	(a)	Discuss the working principle of The Matrix Converter for power electronics circuits.	07	
	(b)	Write a short note on PWM technique for matrix converter. OR	07	
Q.3	(a)	Discuss the basic concept of multi pulse converter. Explain working of 24 pulse converter with neat diagram.	07	
	(b)	Explain how averaged model is generated for buck type dc-dc converter.	07	
Q.4	(a) (b)	Discuss parallel resonant circuit for load resonant inverter. Describe working of capacitor clamped multilevel inverter circuit, OR	07 07	
Q.4	(a)	What is need of small signal model? Explain small signal model of a converter circuit.	07	
	(b)	Discuss various transformer connections for multi-pulse converter.	07	
Q.5	(a) (b)	Discuss about the power electronics switches used in Matrix converter. Explain PI controller with suitable example. OR	07 07	
Q.5	(a) (b)	Write note on hysteresis control for the controller. Explain the average modeling of boost type DC-DC converter circuit.	07 07	
