Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

ME - SEMESTER- II(New course) • EXAMINATION (Remedial) - WINTER- 2015

Subject Code: 2722911 Subject Name: INDUSTRIAL DRIVES Time: 2:30 pm to 5:00 pm Instructions: Total Marks			nte: 09/12/2015	
		70		
11100	1. 2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a) (b)	Discuss mathematical modeling of an AC machine. Explain two quadrant DC motor drive operations in detail.	07 07	
Q.2	(a)	Explain following terms with respect to the controlled converter. (i) Harmonic Factor (ii) Displacement Factor (iii) Input Supply Power Factor	07	
	(b)	The speed of a 10 kW, 230 V, 1200 rpm separately excited dc motor is controlled by a single phase full wave converter. The rated armature current is 38 A & the armature resistance of the motor is 0.3 ohm, as supply voltage is 260 V, motor voltage constant K is 0.182 V/rpm. Find (i) The motor torque. (ii) The speed of the motor. (iii) The supply power factor. For firing angle =30° OR	07	
	(b)	Discuss how the motor efficiency of an inverter fed induction motor varies with frequency.	07	
Q.3	(a)	Explain stator voltage control method for speed control of induction motor. Also discuss why it is suitable for fan type load.	07	
	(b)	Discuss rotor resistance control of induction motor. Also draw its speed Torque characteristics. OR	07	
Q.3	(a) (b)	In Time Ratio Control of buck chopper circuit supplying to the motor load, prove that the ripple in output current will be maximum for 50% duty cycle. Assume motor draws continuous current. Explain reference frame theory in brief.	07 07	
Q.4	(a) (b)	Discuss four quadrant chopper circuit for DC motor. Compare operation of induction motor operated through current source inverter and voltage source inverter.	07 07	
		OR	^ -	
Q.4	(a) (b)	Explain closed loop control of DC motor operated through chopper circuit. Explain indirect vector control scheme for induction motor.	07 07	
Q.5	(a) (b)	Explain Derating of induction motor due to Harmonics present in supply. Compare speed control of DC motor based on chopper and phase control circuit.	07 07	
~ <i>-</i>		OR	^-	
Q.5	(a)	Explain Direct torque control method for induction motor Explain self synchronous operation of synchronous motor drive	07	