GUJARAT TECHNOLOGICAL UNIVERSITY ME - SEMESTER- II(New course) • EXAMINATION (Remedial) – WINTER- 2015

Subject Code: 2724407 Date: 11/1 Subject Name: VLSI in Wireless Communication Systems			2/2015	
Time:2:30 pm to 5:00 pm Total Marks: Total Marks:			70	
	1. 2. 3.	i ,		
Q.1	(a)	Draw heterodyne architecture of RF receiver and also explain the functions of	07	
		Band selection filter, Image rejection filter and channel filter		
	(b)	For noisy two port networks of K- stages, each with noise derive equation for Noise figure	07	
Q.2	(a)	Write short note on types of circuit noise and also mention the effect of these	07	
		noise on over all wireless communication channel.		
	(b)	Explain the operations of BPSK modulator and demodulator with block	07	
		diagrams. OR		
	(b)	Explain the operations of QPSK modulator and demodulator with block diagrams.	07	
Q.3	(a)	Derive the equation of path loss for wireless communication channel.	07	
	(b)	Explain the multipath fading in details	07	
		OR		
Q.3	(a)	Describe short note on additive white Gaussian noise	07	
	(b)	Discuss for receiver design, the effects of non idealities into the corresponding design parameters.	07	
Q.4	(a)	Describe the operation of Ring oscillator using circuit diagram	07	
	(b)	Draw input bias scheme for Wideband LNA & explain in detail	07	
		OR		
Q.4	(a)	Explain with circuit diagram PLL based frequency synthesizer.	07	
	(b)	Compare wide band LNA and Narrow band LNA	07	

1

- Q.5 (a) Draw generalized LNA topology and its equivalent lumped parameters of an 07 amplifier and explain its working
 - (b) Mention in detail : Design steps of Sigma Delta Modulator

OR

- Q.5 (a) Draw the circuit employed to match the load with signal source in an LNA and 07 derive the expression for Zin and comment on it.
 - (b) Explain the operations of FSK modulator and demodulator with block 07 diagrams.

07