

Seat No.: \_\_\_\_\_

Enrolment No. \_\_\_\_\_

# GUJARAT TECHNOLOGICAL UNIVERSITY

M.E. SEMESTER III–EXAMINATION – WINTER 2015

Subject code: 2732903

Date: 04/12/2015

Subject Name: Power Electronics for Power System

Time: 2:30 PM to 5:00 PM

Total Marks: 70

## Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Notations used have usual meaning.

- Q.1** (a) Discuss merits and demerits of AC transmission system. Compare DC versus AC transmission system in all respect. **07**
- (b) Write a detailed note on reactive power compensation in electrical power system. **07**
- Q.2** (a) Discuss about active and reactive power flow control in HVDC transmission system. **07**
- (b) Discuss voltage control by Static VAR Compensator (SVC). **07**
- OR**
- (b) Discuss multiple pulse converter for HVDC transmission system. **07**
- Q.3** (a) Discuss Thyristor controlled reactor (TCR) as a shunt compensator along with its characteristic. **07**
- (b) Write a short note on reference frame theory. **07**
- OR**
- Q.3** (a) Explain the operation of STATCOM with characteristics. **07**
- (b) Discuss the effect of series and shunt compensation schemes on power transfer capacity. **07**
- Q.4** (a) Explain Fixed Capacitor Thyristor Controlled Reactor (FC-TCR) with neat diagram. Discuss its application. **07**
- (b) Discuss how shunt compensation can be achieved with ideal midpoint reactive compensator. **07**
- OR**
- Q.4** (a) Explain working principle of Thyristor controlled series capacitor (TCSC) with neat diagram. **07**
- (b) Enumerate advantages of series compensation. **07**
- Q.5** (a) Write a brief note on advantages and applications of FACT controller. **07**
- (b) Explain Static Synchronous Series compensator (SSSC) with neat diagram. **07**
- OR**
- Q.5** (a) Write a short note on GTO Controlled Series Capacitor. **07**
- (b) Explain the operation of Unified power flow controller (UPFC) with vector diagram. **07**

\*\*\*\*\*