

GUJARAT TECHNOLOGICAL UNIVERSITY**M.E. SEMESTER III-EXAMINATION – WINTER 2015****Subject code: 2734203****Date: 04/12/2015****Subject Name: High Speed CMOS VLSI Circuit****Time: 2:30 PM to 5:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain inter-Die variation in detail. 07
 (b) List out Fail causes and explain it. 07
- Q.2** (a) Find the Elmore delay the nodes Vout3 and Vout4 in the RC tree shown in Fig. 1. 07
 (b) Calculate the Elmore delay from In to Out1 and from In to Out2 from fig.2. Which one is critical path? Assume $R = 100\Omega$ and $C = 10\text{fF}$. Calculate the Elmore delay of the critical path that you found. 07
- OR**
- (b) Explain power optimization for high speed VLSI circuit. 07
- Q.3** (a) Explain Static CMOS Structure in detail with diagram and its type. 07
 (b) Explain Domino CMOS in detail with diagram. 07
- OR**
- Q.3** (a) Explain Self-Resetting Domino Structure (SRCMOS) on detail. 07
 (b) Explain differential Domino Structure with diagram. 07
- Q.4** (a) Explain Clocked Pass –Gate Logic in detail with diagram and its type. 07
 (b) List out Latched Domino structure and explain Simple set Differential logic (SSDL). 07
- OR**
- Q.4** (a) List out latching single-ended logic types and explain double edge triggered flip-flops (DETFF) with necessary diagrams. 07
 (b) Write a short note on latch clocking. 07
- Q.5** (a) List out latching single-ended logic types and explain Differential cascode voltage switch(DCVS) latch with necessary diagrams 07
 (b) Write a short note on race free latches for Pre charged logic. 07
- OR**
- Q.5** (a) Explain Circuit optimization techniques for high speed VLSI circuit. 07
 (b) Explain any one mathematical optimization techniques. 07

 


Fig.1

 


Fig.2